

A Fully-Integrated 5GHz CMOS Wireless-LAN Receiver

Hirad Samavati

Center for Integrated Systems
Stanford University


Outline

- Motivation
- Introduction to Wireless LAN
- Receiver Architecture
- Circuit Implementations
- Offset Cancellation Techniques
- Fractal Capacitors
- Measurements
- Conclusions


Motivation

- Demand for wideband wireless local area network (LAN)
 - High data rate ($> 20\text{Mb/s}$)
 - Low cost (CMOS)
 - Low power
- New released frequency band in US
 - Unlicensed national information infrastructure (U-NII) band
- Existing frequency band in Europe
 - High performance radio LAN(HIPERLAN) band

Available Frequency Bands

 

- U-NII and HIPERLAN frequency bands.

 

- Proposed channel allocation for a U-NII band WLAN system.
 - Compatible with HIPERLAN.

HIPERLAN Receiver Requirements

Modulation	GMSK
Maximum signal level	-25dBm
Sensitivity	-70dBm
Channel bandwidth	23.5MHz
Spurious emissions 30MHz-1GHz 1GHz-25.5GHz	-57dBm -47dBm


$$NF < -143.7\text{dBm/Hz} - 12\text{dB} - (-174\text{dBm/Hz}) = 18.3\text{dB}$$

↑
Sensitivity
(-70dBm)/(23.5MHz)


↑
Pre-detection SNR

↑
Available noise power of the antenna


Receiver Architecture

 

LO Frequencies


 


- Image signal is small.

 

- LO_2 easily obtained from LO_1 .



Image Rejection

  

- Series resonance @ f_{img} → improves image rejection

Noise Rejection

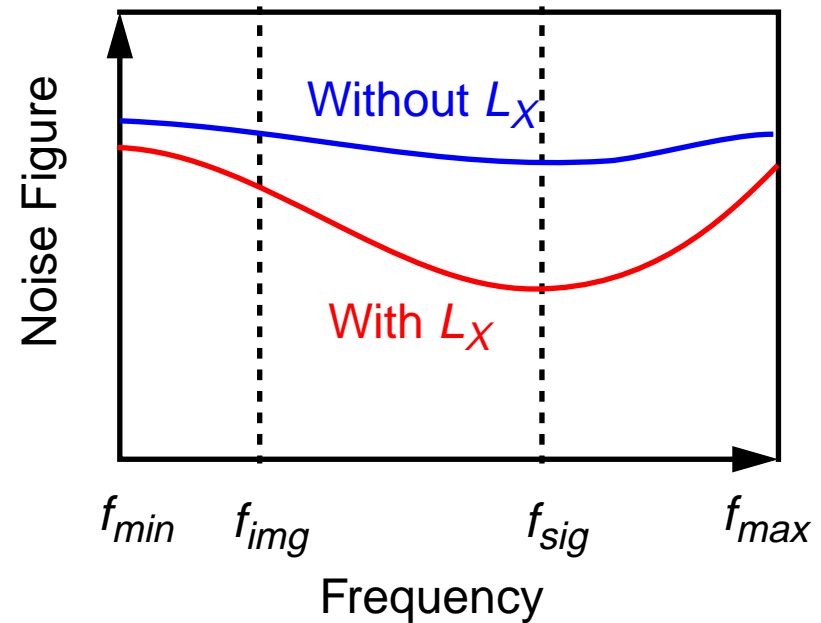 Parasitic capacitance C_x degrades the noise performance.



- Parallel resonance @ f_{Sig} → improves noise figure


Solution: Third-Order Filter

$$Z_f(s) = \frac{L_5 \cdot (C_3 + C_1) \cdot s^2 + 1}{C_1 \cdot C_3 \cdot L_5 \cdot s^3 + C_3 \cdot s}$$




$$\omega_p = 0$$

$$\omega_p = \pm \frac{1}{\sqrt{L_5 \cdot C_1}}$$


 
$$\omega_z = \pm \frac{1}{\sqrt{L_5 \cdot (C_3 + C_1)}}$$




LNA/Filter Transfer Function

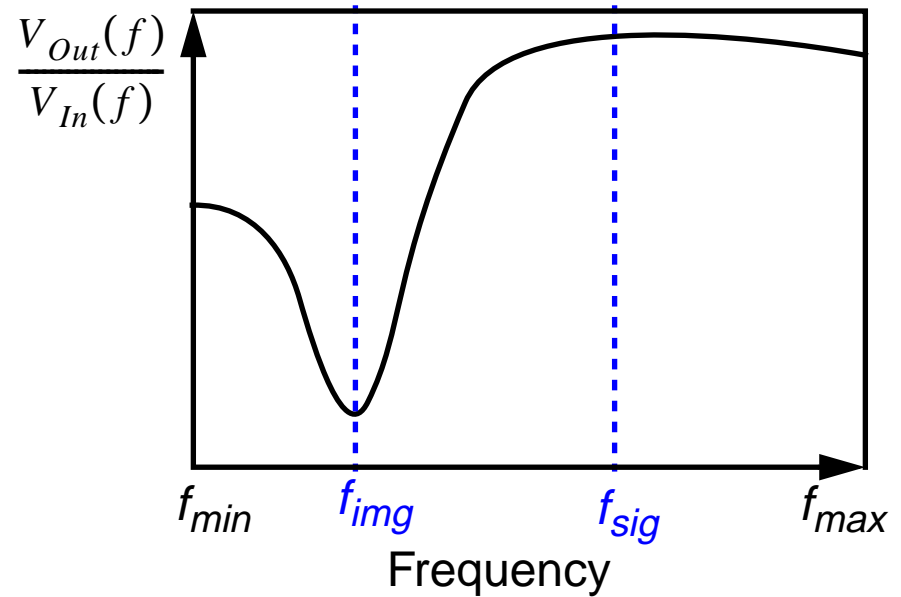  


Equivalent Noise Circuit for the LNA

  

Filter Noise Model

 

Simplifies to

 

Noise Formulas

$$F_{no-filter} = F_1 + 4R_s \gamma_3 g_{do3} \left(\frac{\omega_0^2}{\omega_T} \right) \left(\frac{C_x^2}{g_{m3}} \omega_0^2 \right)$$


$$F_{with-ideal-filter} = F_1$$

$$F_{tot} = F_1 + \Psi \cdot 4R_s (\gamma_5 g_{do5} + G_{L5}) \left(\frac{\omega_0^2}{\omega_T} \right)$$


Where $\Psi = \frac{C_3^2 \cdot \omega_0^2}{\left(\frac{C_3^2}{C_x + C_3} \right)^2 \cdot \omega_0^2 + (G_{L5} - g_{m5})^2}$,

and F_1 is the noise figure of the first stage defined in: D. Shaeffer and T. Lee, "A 1.5V, 1.5 GHz CMOS Low Noise Amplifier", *IEEE Journal of Solid-State Circuits*, May 1997, pp. 745-759.


Receiver Architecture

 


Circuit Implementation: LNA and filter

 

Receiver Architecture

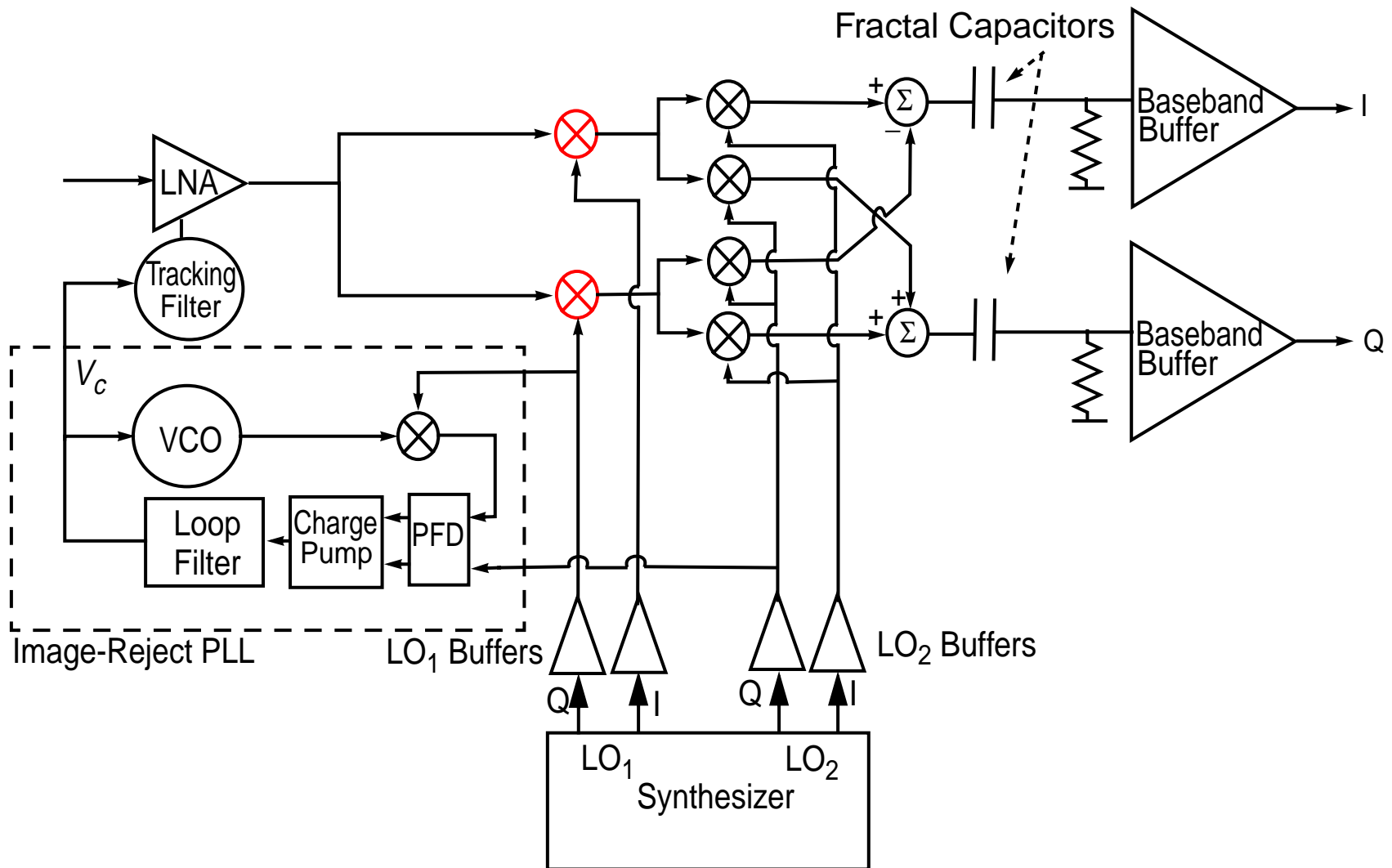


Circuit Implementation: First Mixers

 


- A. Shahani, et al, "A 12-mW wide dynamic range front-end for a portable GPS receiver," *IEEE J. Solid-State Circuits*, vol. 32, pp. 2061-2070, Dec. 97.


Receiver Architecture

 

 
Circuit Implementation: VCO and Loop Mixer





Receiver Architecture

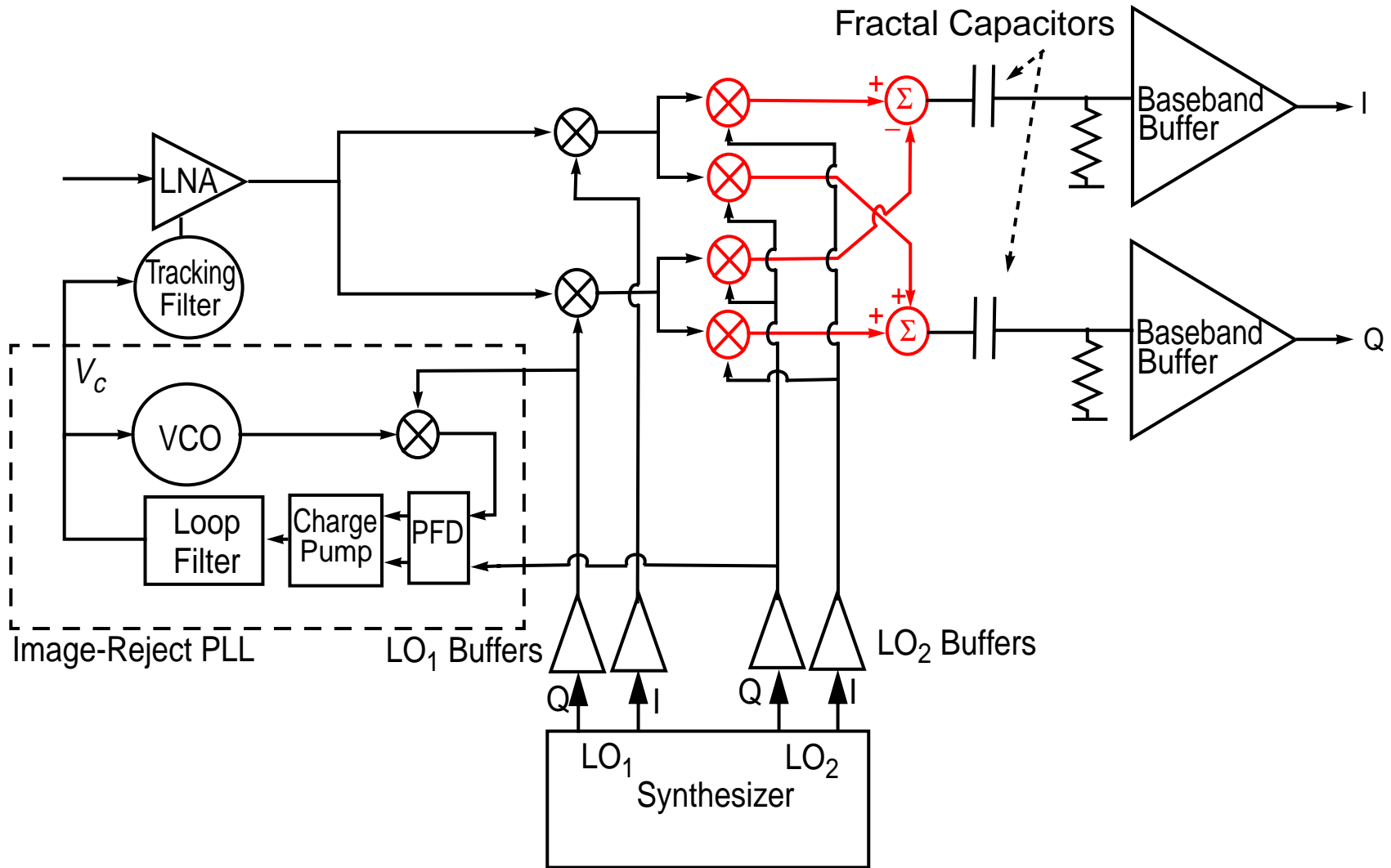

Circuit Implementation: Second Mixers

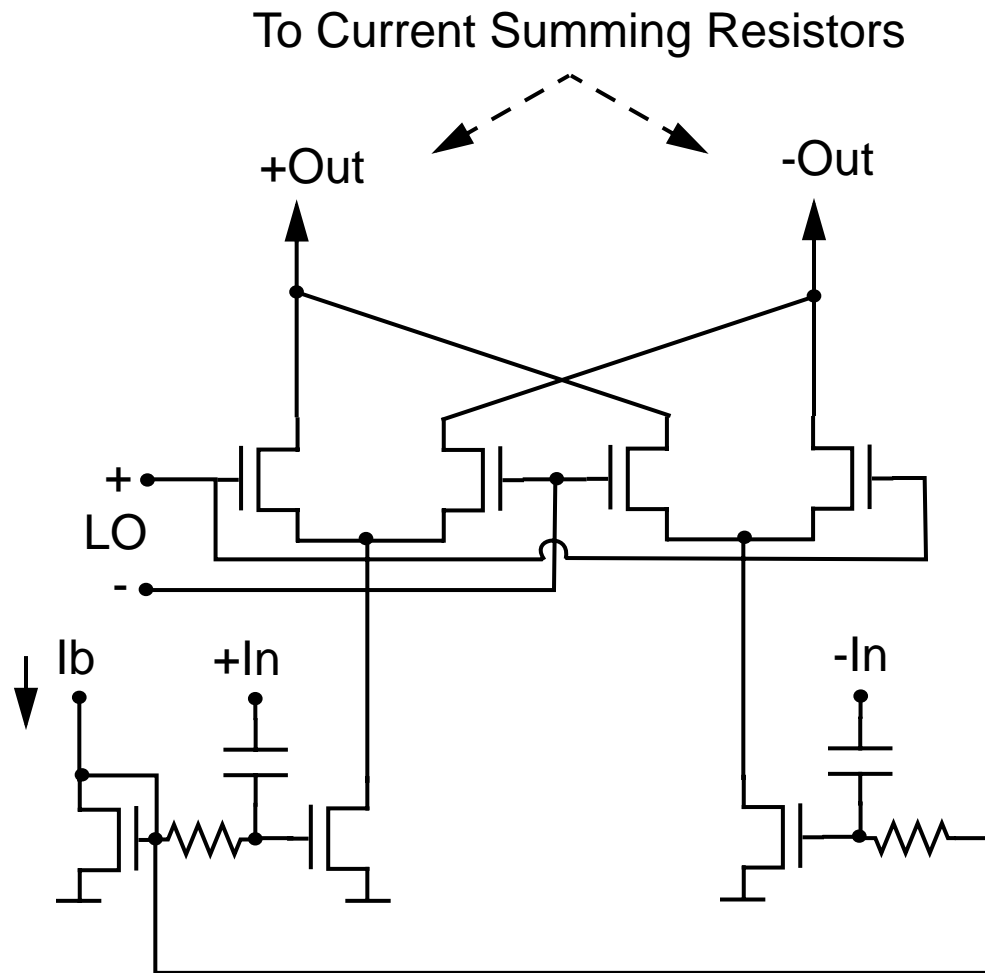


DC Offsets

  

DC Offset Cancellation Techniques


- Capacitive Coupling

- Requires a large capacitor

 


- Negative Feedback

- Nonlinear

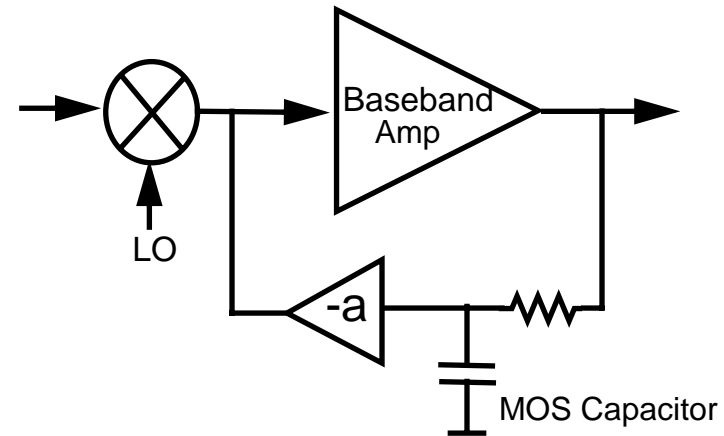

- TDMA offset Cancellation

- Requires a large capacitor

 

Traditional Capacitors

- **Gate Capacitance:**

- High capacitance per unit area
- Nonlinear
- Requires DC bias voltage
- Low breakdown voltage
- Medium Q

- **Junction Capacitance:**

- Highly nonlinear
- Requires DC bias voltage
- Sensitive to process variations
- Low Q
- Large temperature variation

- **Metal to Metal / Poly Capacitance:**


- Linear
- High Q
- Small temperature variation
- Low capacitance per unit area

- **Thin-Insulator Capacitors:**


- Linear
- Expensive
- Not available in standard CMOS

Improving Capacitance Density

 
- Lateral flux improves capacitance density.



 - Structures with large periphery are desirable.
- Some fractals have finite area but infinite perimeter.




Fractal Capacitor

 

of cross-connected layers=4
Horizontal spacing= $0.6\mu\text{m}$
Vertical spacing= $0.8\mu\text{m}$
Capacitance boost factor=2.3


Scalability

 - Unlike conventional parallel-plate structures, the capacitance per unit area increases as the process technologies scale.




Reduction of the Bottom-Plate Capacitance

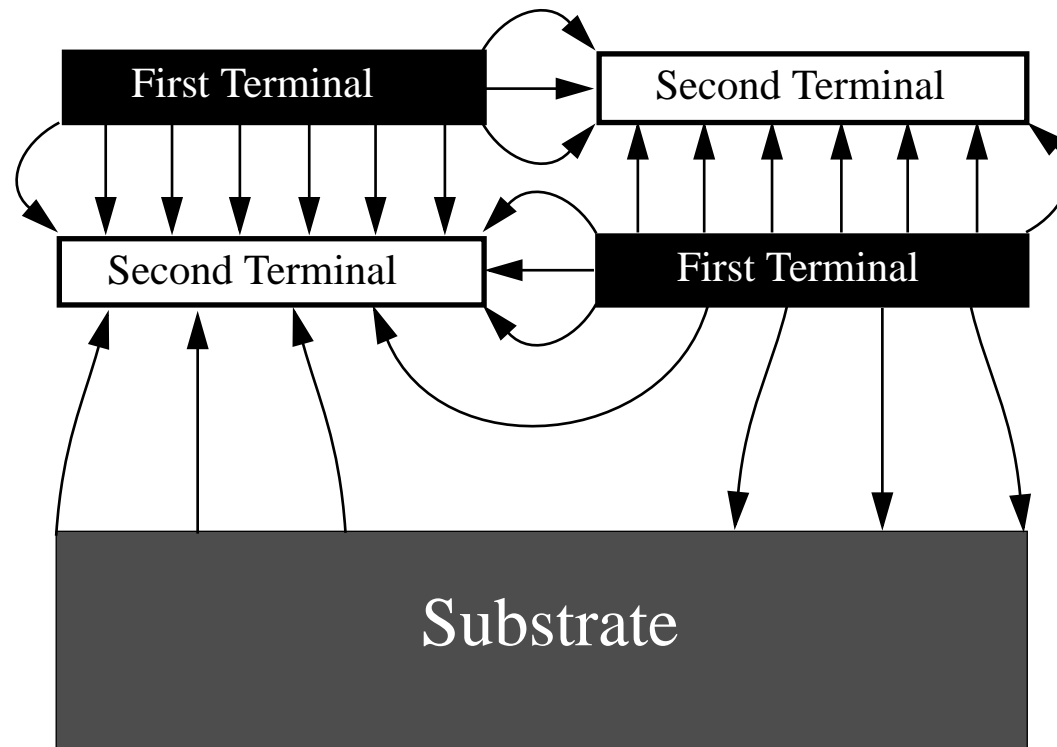- Area is smaller.
- Some of the field lines terminate on the adjacent plate instead of the substrate.




Improved Matching

 

Capacitance distribution across the wafer


CAD Tool

 


LGFC

Layout Generator for Fractal Capacitors

Receiver Architecture

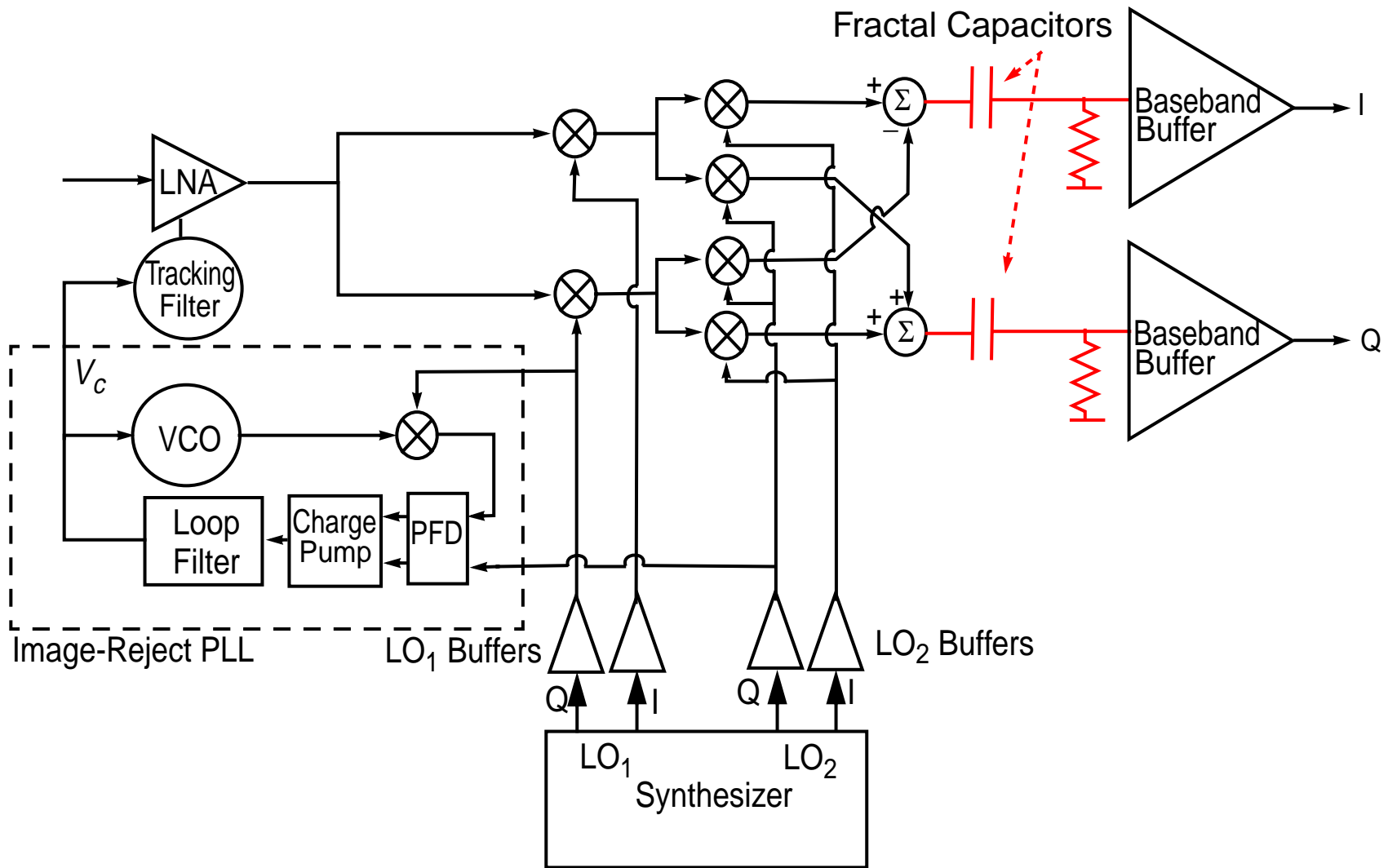

Offset Cancellation Circuit

 

Capacitor

Area: $131 \times 165 \mu\text{m}$

Capacitance value: 15pF

Bottom-plate capacitance/terminal: 1.2pF

Self-resonance frequency: 11.3GHz

Capacitance density: $700 \text{aF}/\mu\text{m}^2$


Capacitance boost factor: 3.5

Resistor


Area: $103 \times 61 \text{mm}$

Resistance value: $2.1 \text{M}\Omega$

Bottom-plate capacitance/terminal: 0.3pF

 


Die Micrograph

 


Die Area: 4mm^2
Technology: $0.24\text{-}\mu\text{m}$ CMOS


Measured Receiver NF

 


Measured Image Rejection

 


IP3 Measurement Results

 


1-dB Compression-Point Measurement

 

1-dB Blocking Desensitization Point

 

Measured S11 of the Receiver

 

Measured Performance Summary

<i>Signal path performance</i>	Achieved	Required
Noise figure	7.2dB	18.3dB
Voltage gain	26dB	
S_{11}	< -14dB	
Image rejection (filter only)	16dB	
Image rejection (total)	53dB	
Input-referred IP3	-7dBm	
1-dB compression point	-18dBm	-21dBm
LO ₁ Leakage to RF	-87dBm	-47dBm
LO ₂ Leakage to RF	-88dBm	-57dBm
<i>Power dissipation</i>		
Synthesizer	25.3mW	
Divide-by-8 (for LO ₂)	6.0mW	
Signal path	18.5mW	
Image-reject PLL	3.1mW	
LO buffers	5.0mW	
Biasing	0.9mW	
Total power	58.8mW	
Supply voltage	1.8V	
<i>Implementation</i>		
Die area	4mm ²	
Technology	0.24- μ m CMOS	
Package	32-pin ceramic flat pack	

Contributions

- Implementing the first 5GHz CMOS wireless-LAN receiver.

The receiver is:

- highly integrated
 - low power
 - highly linear and tolerates large blockers
- Developing a novel RF filter topology that:
 - rejects the image signal
 - improves the LNA noise figure
 - Demonstrating the feasibility of automatic tuning techniques at RF frequencies using a low power image-reject PLL.

Contributions

- Implementing a novel capacitor structure using fractal geometries.
- Demonstrating the benefits of fractal capacitors including:
 - area efficiency
 - linearity
 - scalability
 - reduced bottom-plate capacitance
 - improved matching characteristic
- Developing a CAD tool to automatically generate custom fractal layouts.