

A CMOS Multi-Gb/s 4-PAM Serial Link Transceiver*


March 11, 1999

Ramin Farjad-Rad
Center for Integrated Systems
Stanford University
Stanford, CA 94305

***Funding from LSI Logic, SUN Microsystems, and Powell foundation**



Goals

 

- Networking high-speed (5 -10Gbps) systems for ranges up to 10 meters at lower cost and complexity
 - Parallel buses are costly for long distances.
 - Optical fibers are not beneficial for such small ranges.
 - Serial links on copper cables are an attractive solution for this kind of application.
- Push bandwidth limitations of CMOS serial links
 - CMOS technology is getting cheaper, faster, and more available.
 - Integrate more digital functions on-chip.


Outline

✓ ***Challenges***

- ❑ **System Architecture**
- ❑ **Circuit Implementation**
- ❑ **Test Results**
- ❑ **Conclusion**


Challenges: Interconnection Bandwidth

 - Frequency-dependent attenuation in electrical links due to skin effect resistance and dielectric loss.
 - The -3dB BW of 10-meter PE-142 coax is ~1.0GHz.




Challenges: Interconnection Bandwidth

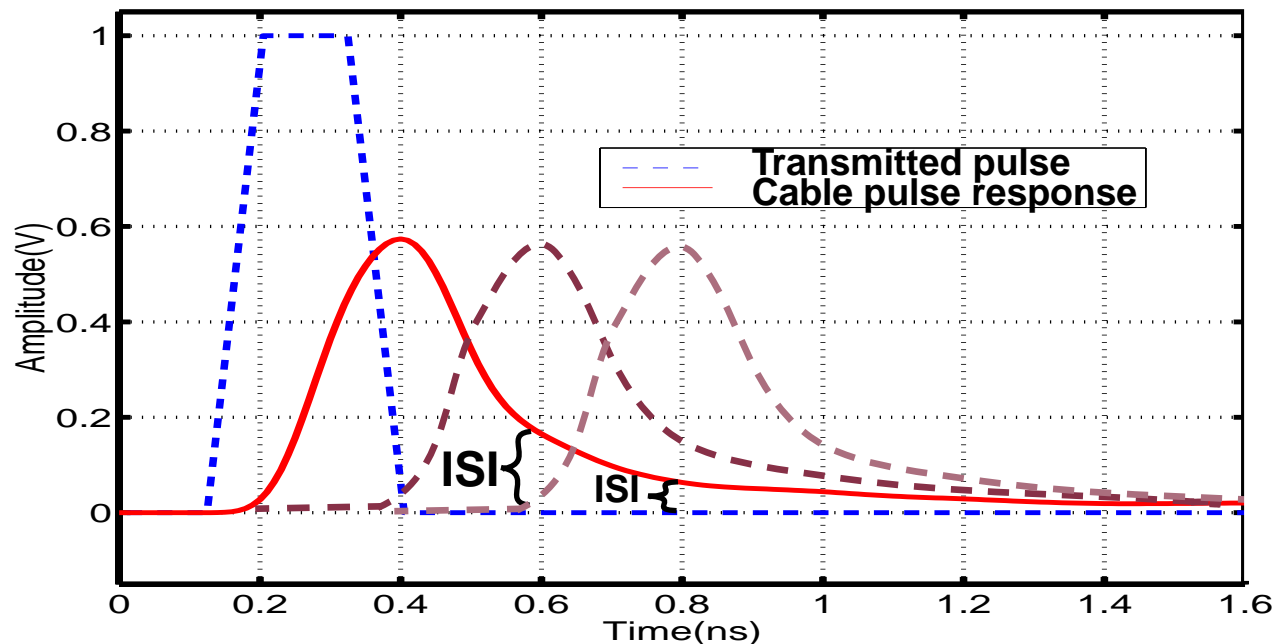- Frequency-dependent attenuation causes ISI.
 - Only channel eigen-waveforms result in no ISI.
 - Generation and detection of true eigen-waveforms is not feasible due to circuit limitations at high frequencies.
 - Trapezoidal pulses are instead used as basis waveforms.
 - Higher symbol rate results in more ISI.



Challenges: Data Generation/Detection

 - Hard to operate CMOS circuits at directly multi-GHz speeds
→ Better to reduce the on-chip frequency
- Recovering embedded timing information from the serial data




- Large frequency variations of on-chip oscillators and small frequency capture range of phase detectors
- Data detection at high speeds
→ Input voltage offset, cross-talk, and signal reflection (reflection ISI) limits the minimum detectable signal.

Outline

- Challenges
- System Architecture***
- Circuit Implementation
- Test Results
- Conclusion

Reduction of On-Chip Frequency

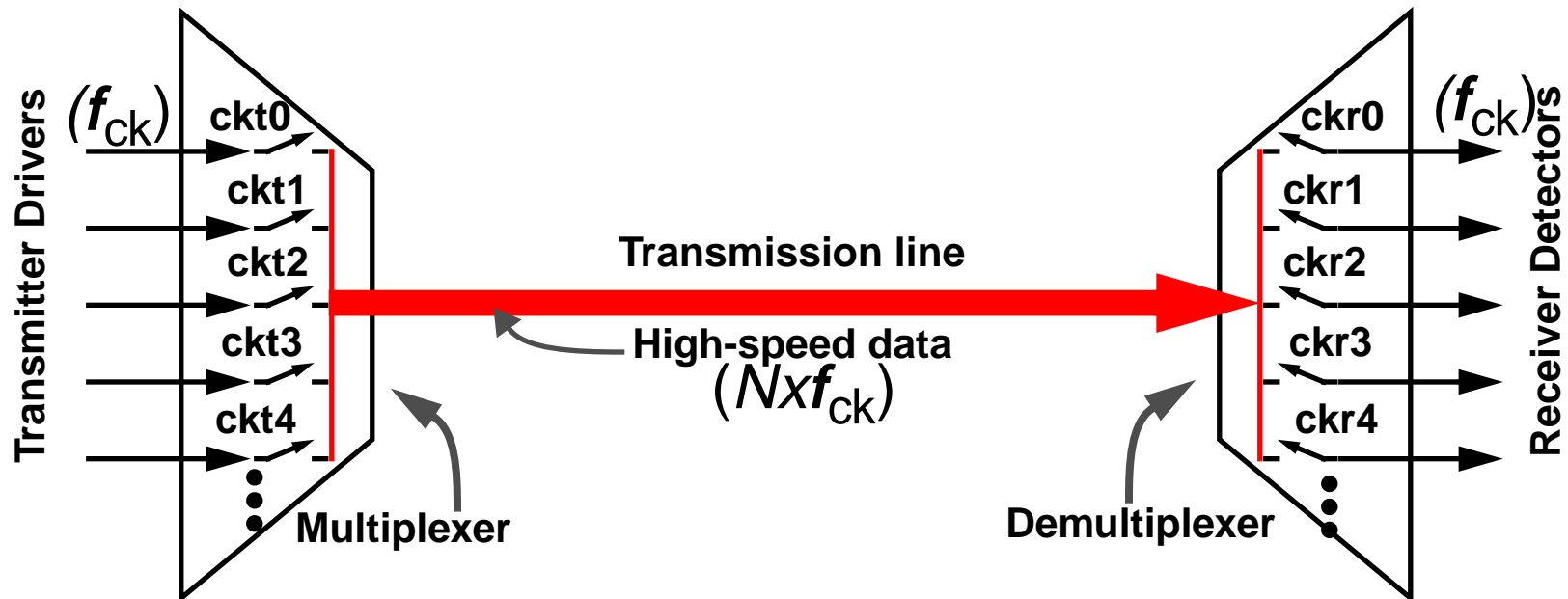
- Multiplexing ($N:1$) and demultiplexing ($1:N$) the high-speed data at the transmission line*
 - Reduces the on-chip frequency by a factor of N
 - For example: $N = 5 \Rightarrow$ (for 5Gsym/s) $f_{ck} = \frac{5G}{5} = 1\text{GHz}$
 - Max switching speed of the process is the limit
CMOS provides high-speed transistor switches



*C-K. Yang, R. Farjad, M. Horowitz, VLSI Symp. 97

Proposed Modulation

- 4-PAM is used for data communication in the serial link
 - Symbol rate reduces to half that of binary transmission.
 - Lower symbol rate reduces ISI and on-chip clock frequency.
 - Higher level PAM was not used because of:
limited transmitter swing, minimum detectable signal
and reflection ISI.
- 4Sym-->5Sym conversion guarantees clock recovery
- Gray code mapping of levels reduces BER by 25% vs.
linear mapping

 


Proposed Architecture to Combat ISI

- To cancel the long tail of pulse response, a pre-emphasis symbol-spaced 2-tap FIR filter is implemented at the transmitter:

$$V_o(n) = V_i(n) - a \cdot V_i(n-1) - b \cdot V_i(n-2)$$


- To sharpen the signal transition edges, a half-symbol-spaced 1-tap high-pass equalizer is implemented at the receiver
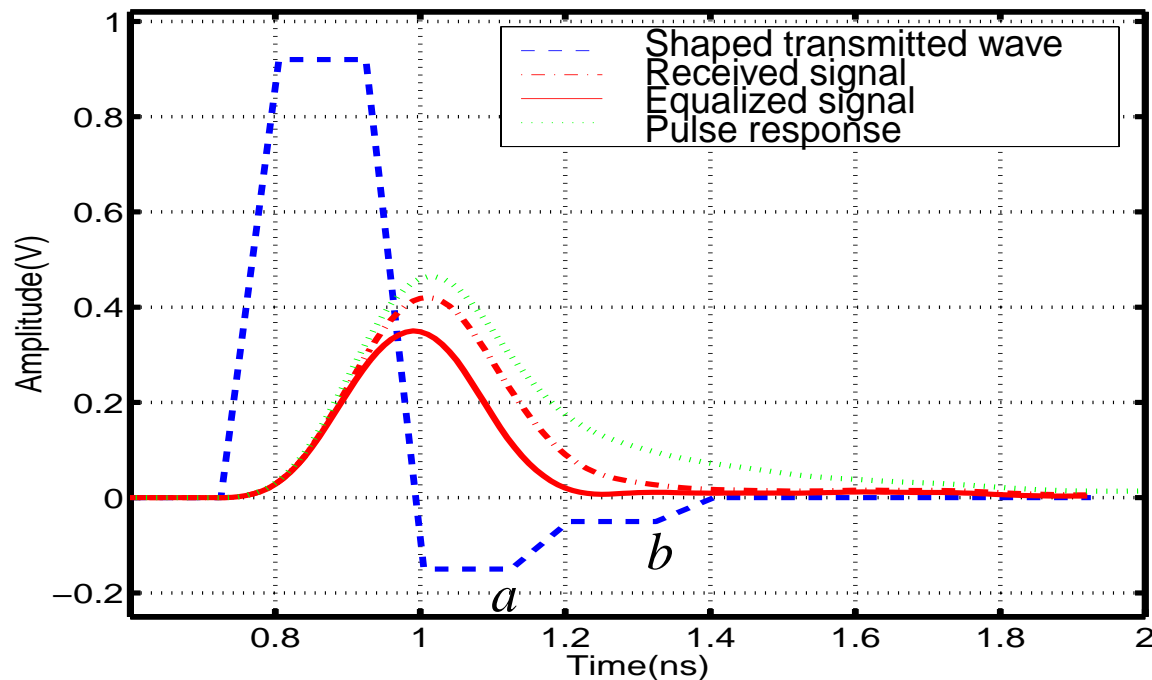
$$V_{eq}(n) = V_i(n) - \alpha \cdot V_i\left(n - \frac{1}{2}\right)$$




Receiver Equalizer

 
- The half-symbol-spaced filter boosts frequency components up to $f = \frac{1}{T_s}$



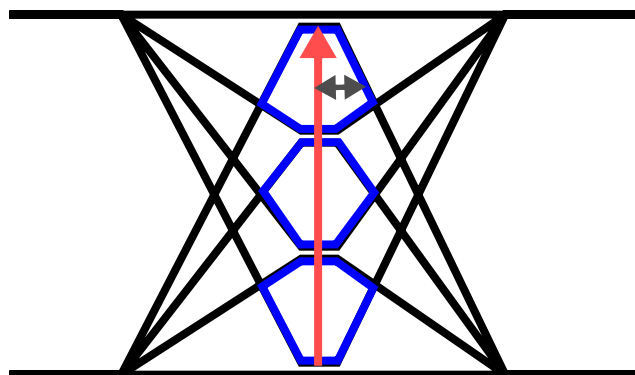- Sharpening the transitions increases the eye opening width.
=>Less sensitive to sampling phase errors.



Slow transition

 


Sharp transition


Outline

- Challenges
- System Architecture
- Circuit Implementation**
- Test Results
- Conclusion

Top Level Architecture

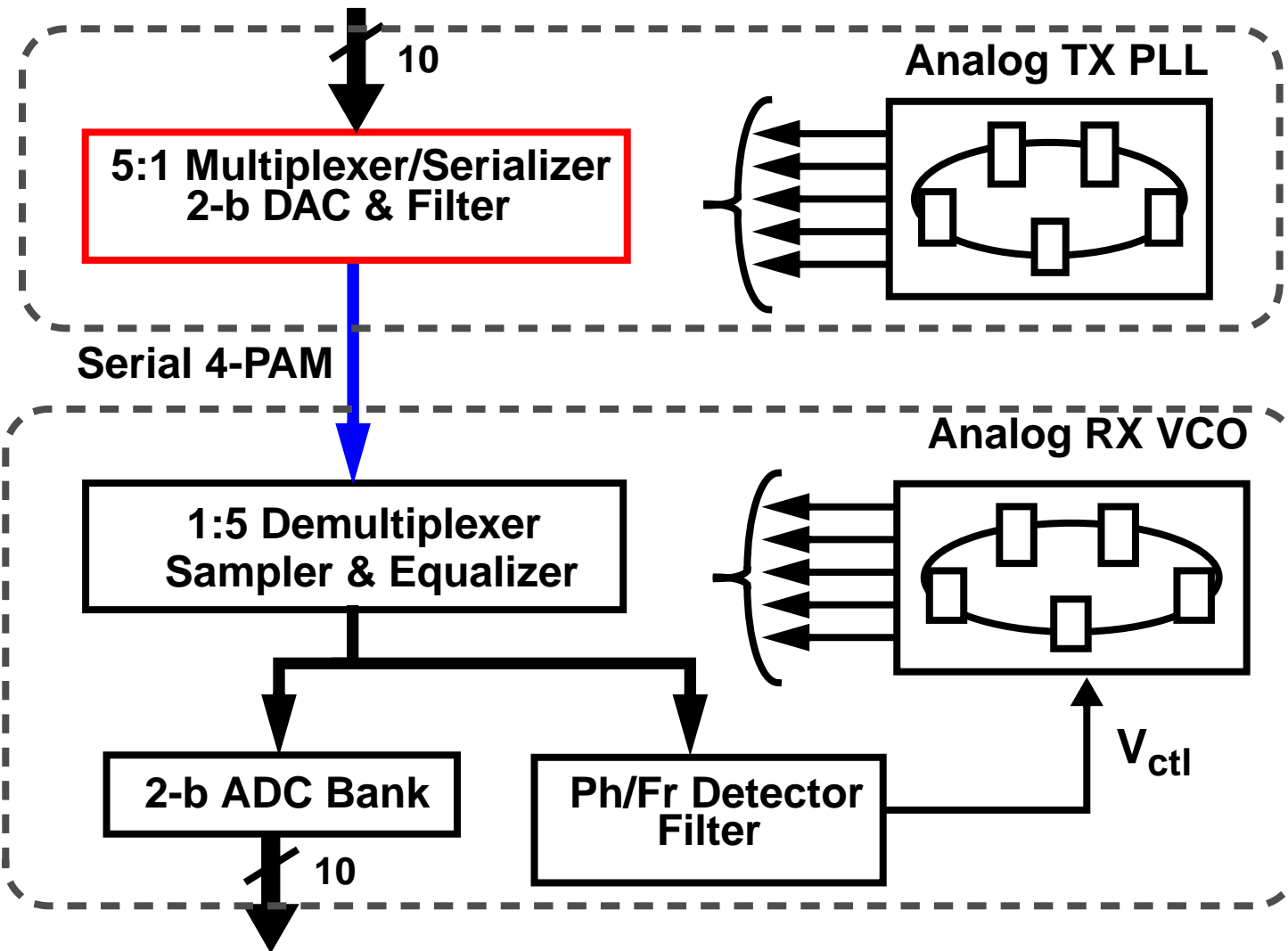


5:1 Multiplexing Transmitter

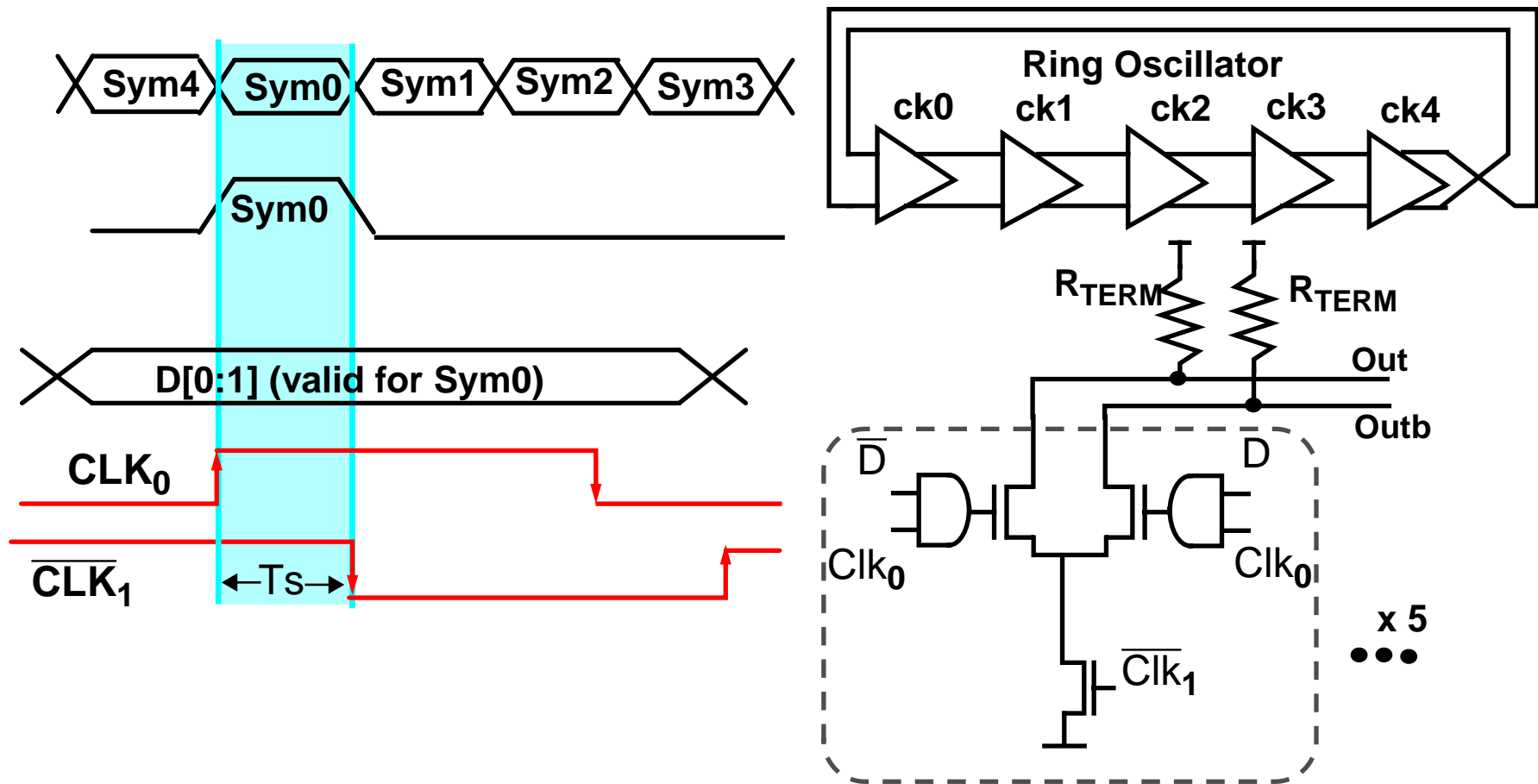


- Each symbol is generated by the rising and falling edges of two phases of clock

2-bit Output Driver

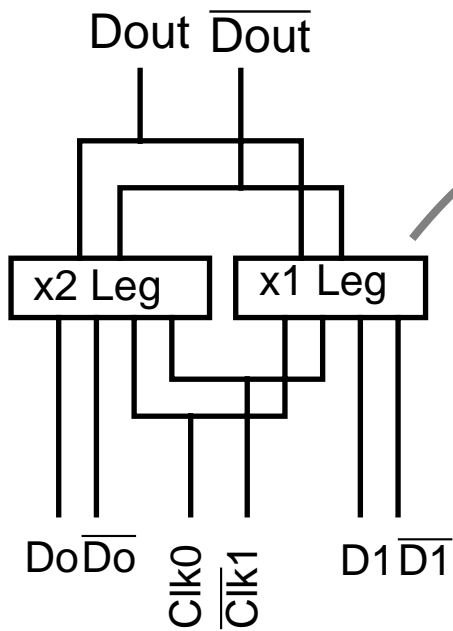


2-bit DAC module

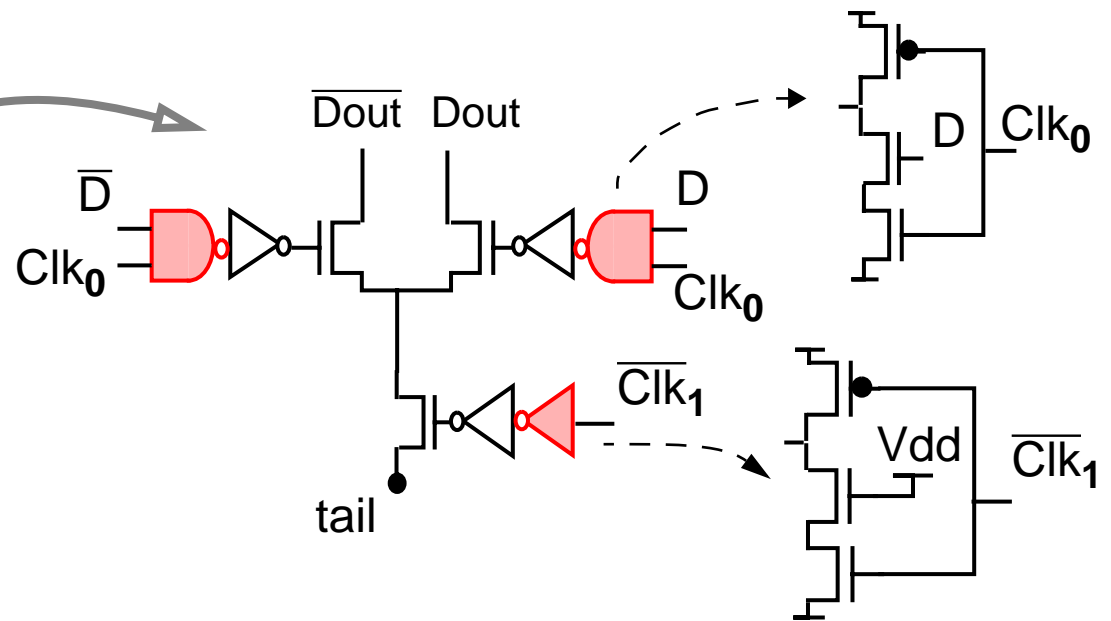


Differential drive leg

4-PAM Preshaping 5:1 Multiplexer

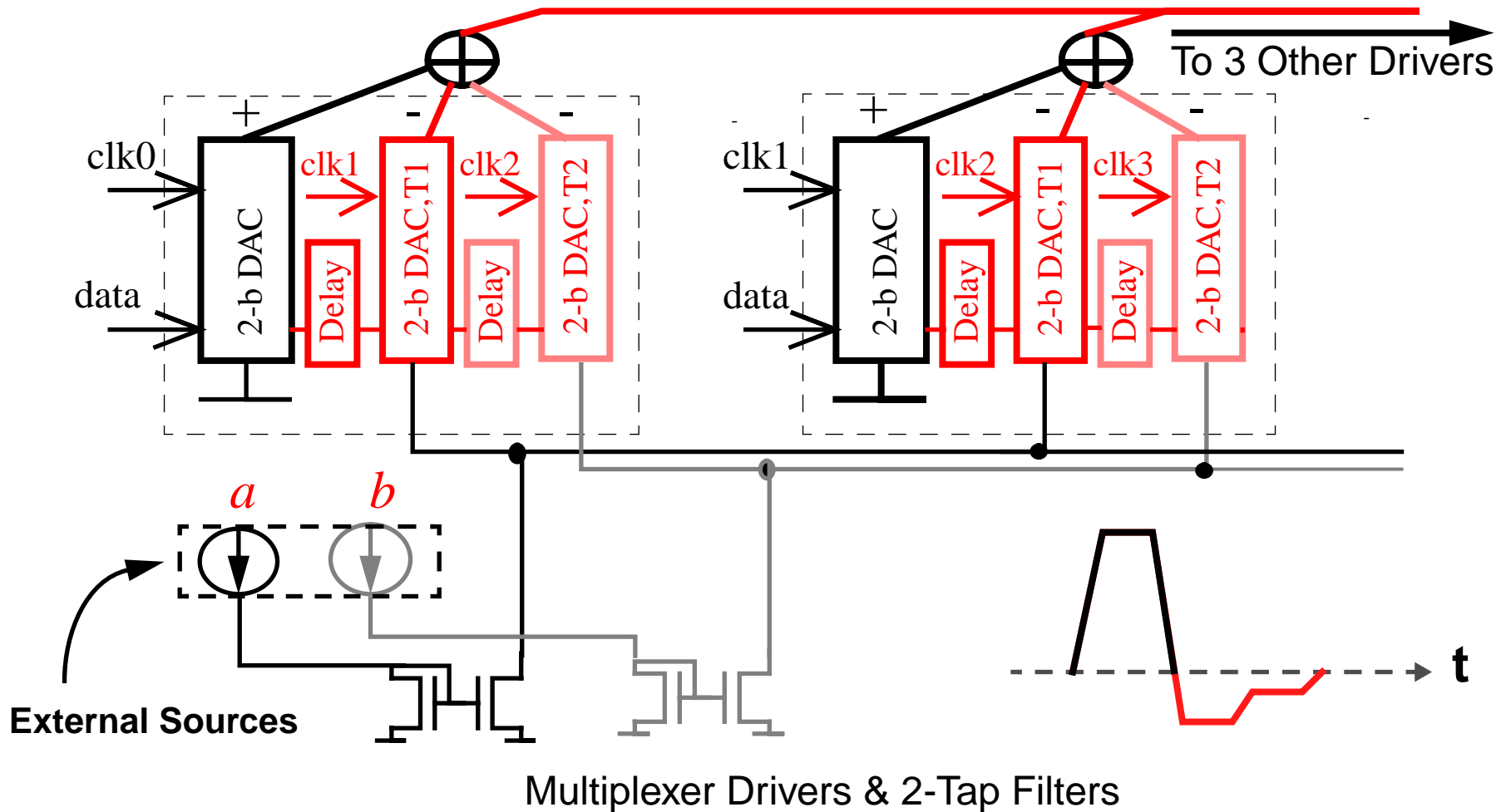

- Each driver generates a filtered symbol independent of other drivers.
- Simple architecture to implement the filter.

Symbol Generation

 


Tap-Drivers timing


Symbol-Width Problem

- Variations in PMOS to NMOS strength ratio result in duty cycle error in the clocks (unbalanced falling & rising times)

 
→ The effective width of the final output symbol decreases.



Pulse-Width Control Loop

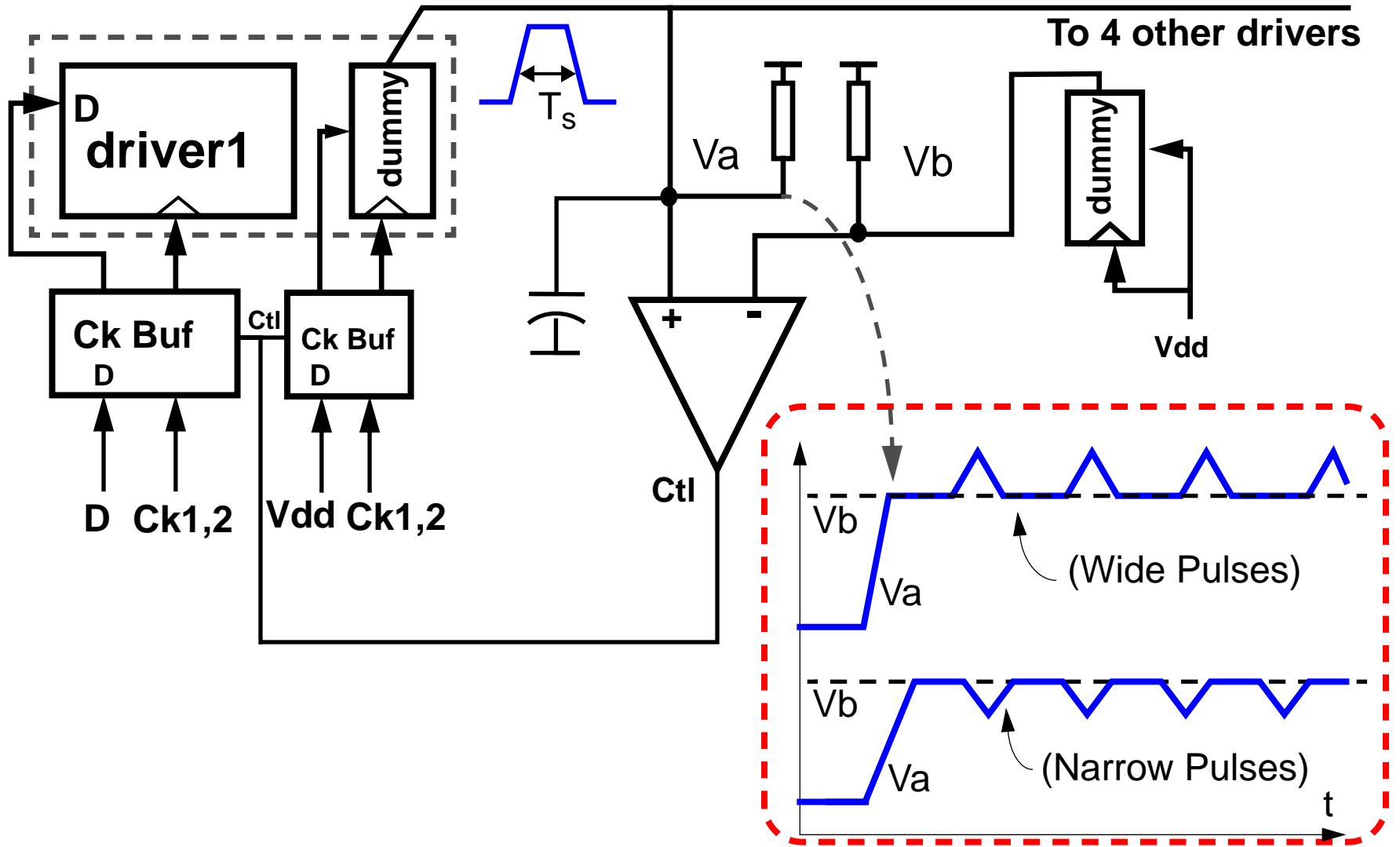


Receiver Timing Recovery

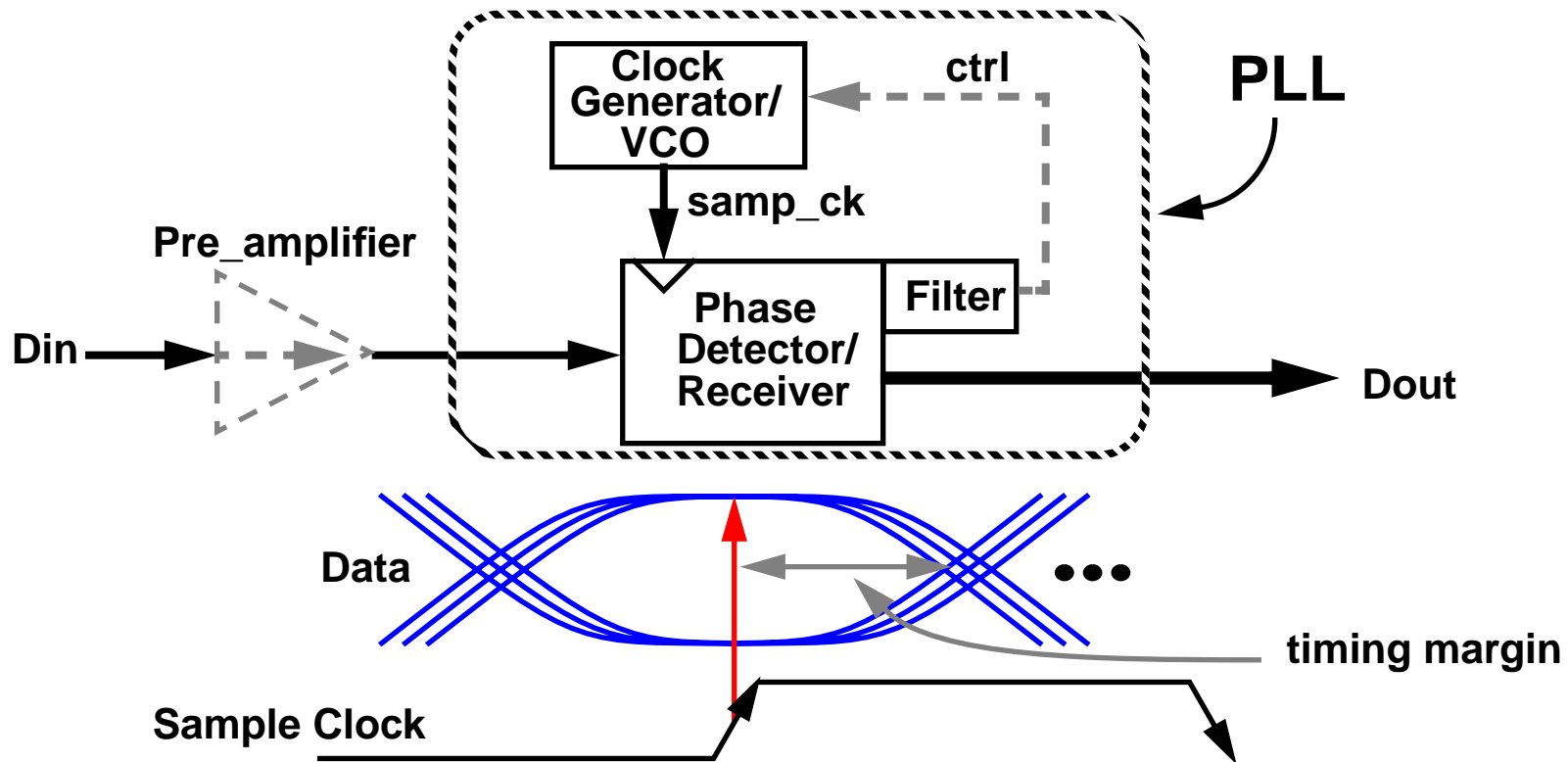


- Oversampling phase detection
 - Many input samplers, Phase quantization error, Complex logic.
- Tracking phase detection
 - Conventional bang-bang control: Low loop bandwidth and capture range
 - Proportional control: Desirable

Top Level Architecture

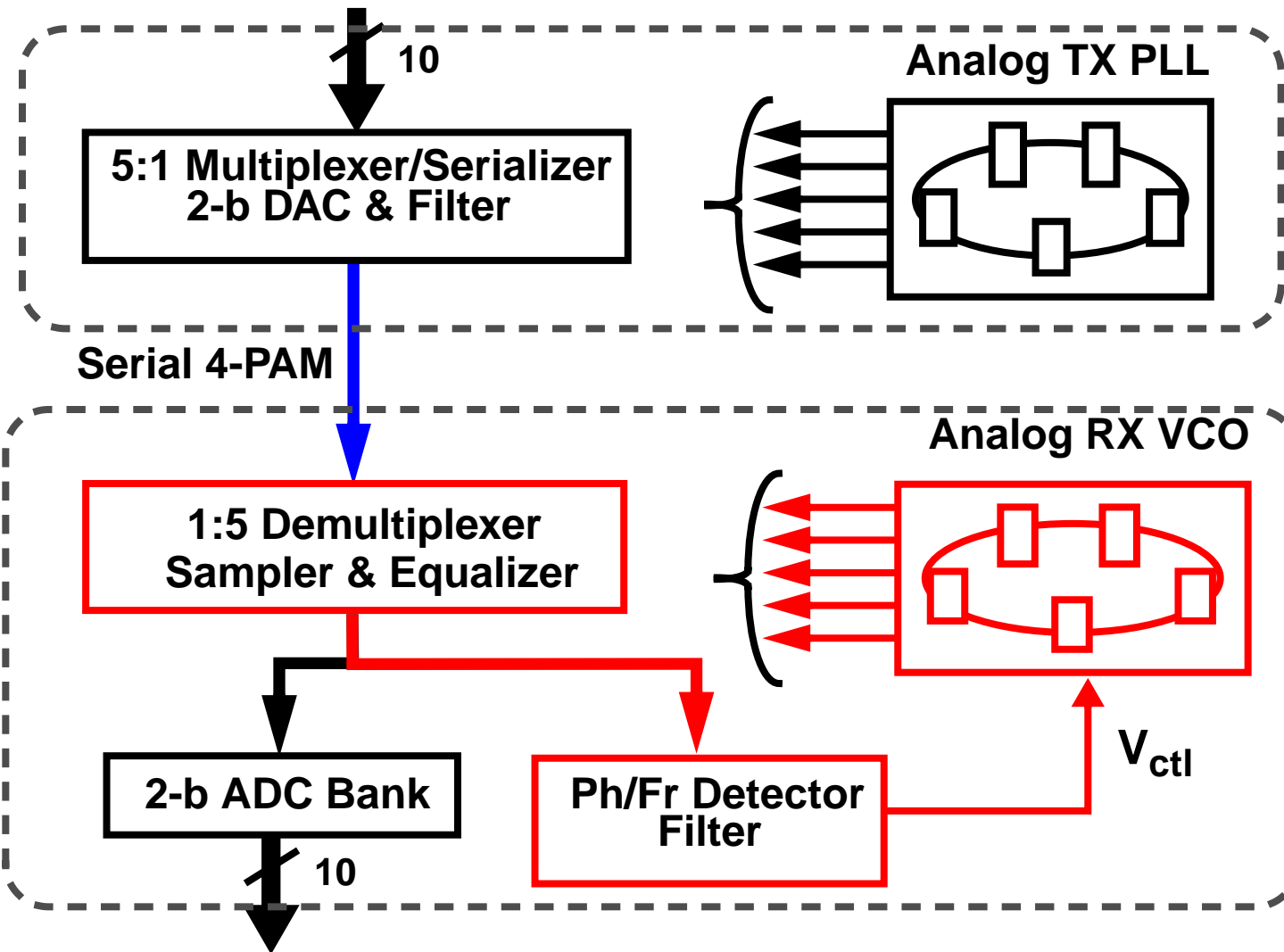


Timing Recovery: Front-end

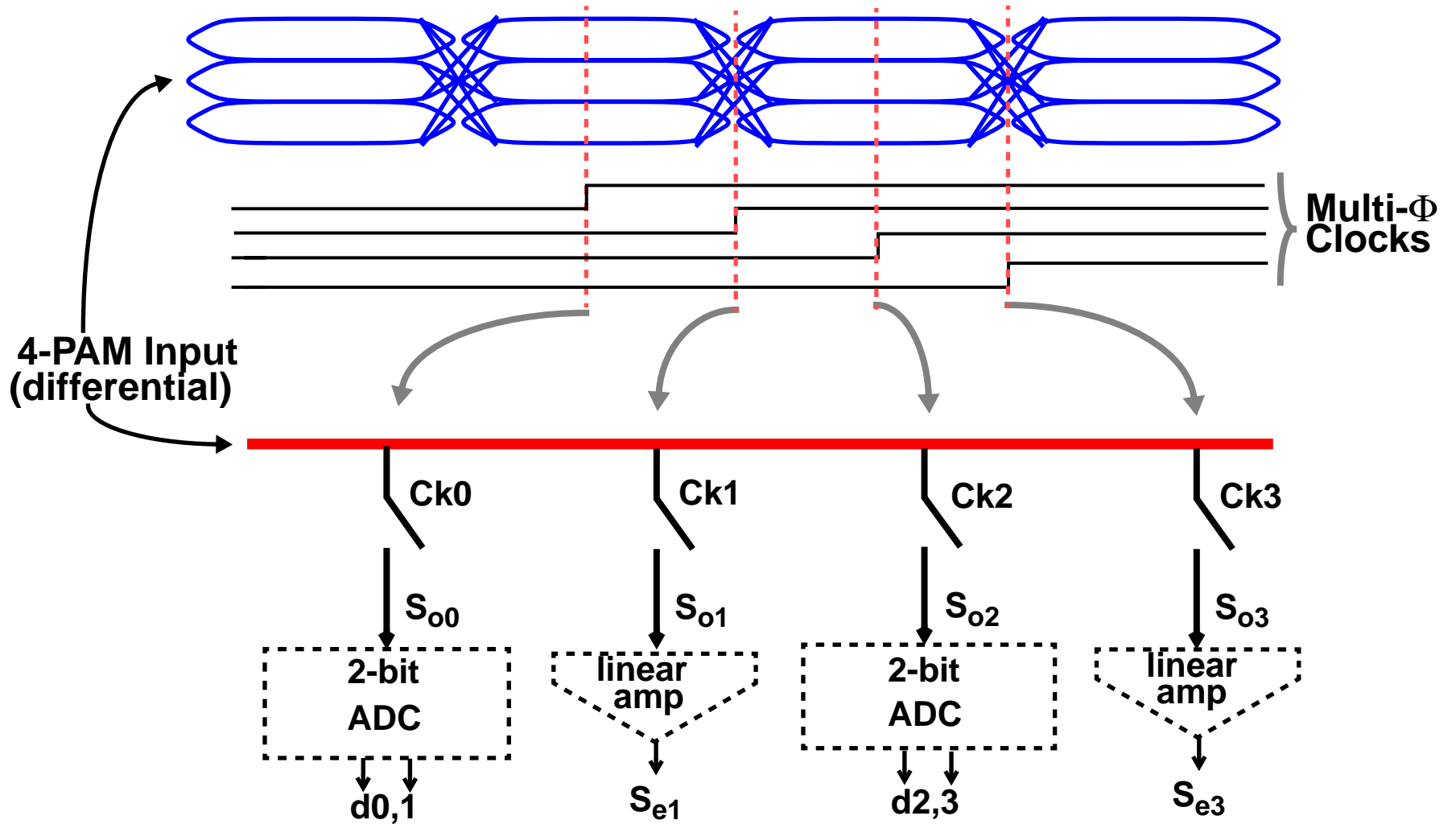

Simplified receiver front-end (x2 oversampling)

Proposed Proportional Phase Detection

 


- Advantages:

- Larger PLL bandwidth and stability compared to bang-bang PLLs.
- Zero systematic phase offset (same detection mechanism for edges and data).
- Zero ripple on control voltage of PLL (unlike bang-bang).

- Disadvantage:


- Voltage offsets of edge samplers translate into phase error.

Three 4-PAM Transitions

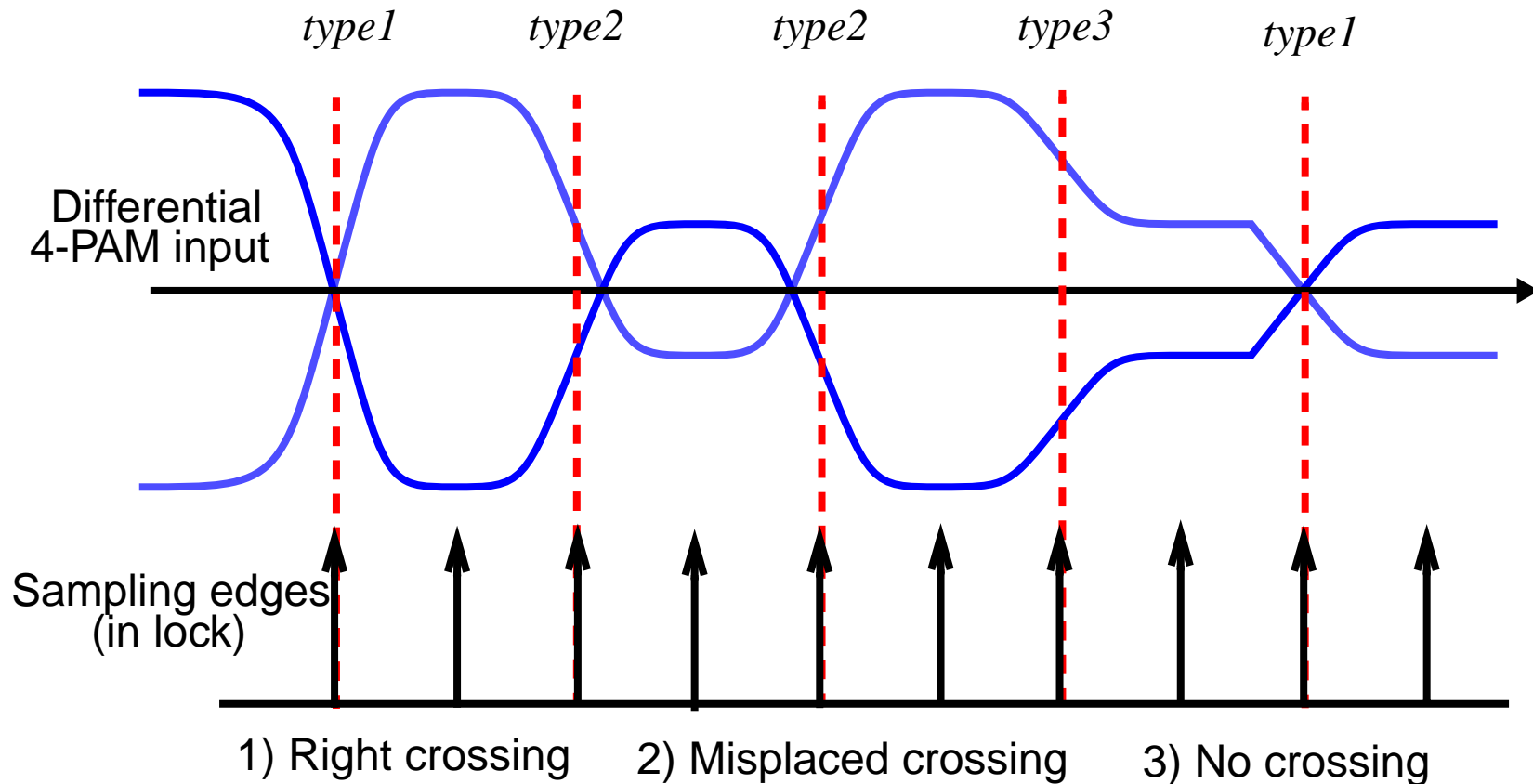

- Only ***type1*** transitions are used for clock recovery
- Transitions ***type2*** and ***type3*** are ignored by a decision logic


Data Phase Detector

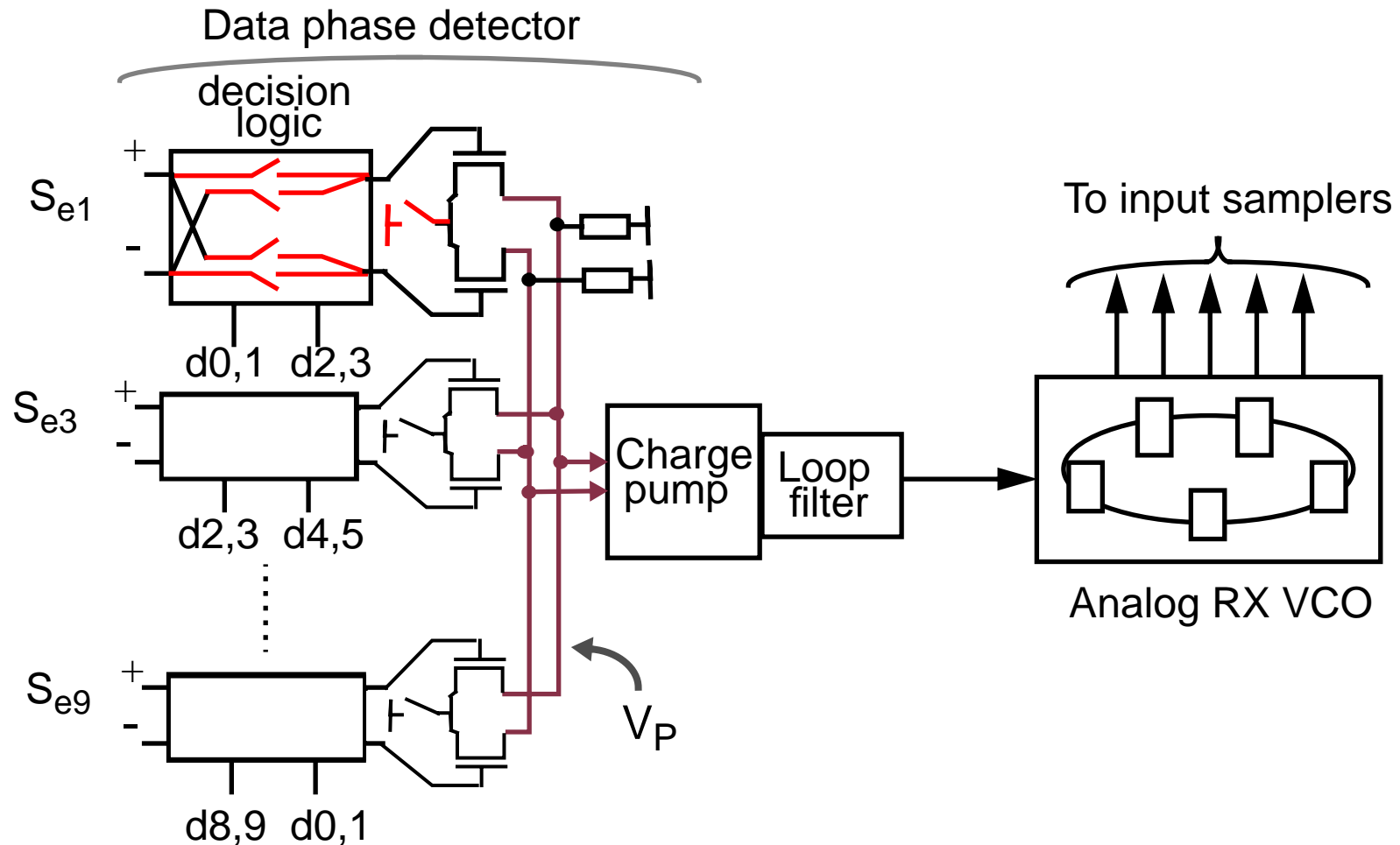


- Edge sample values, S_e , of *type1* are summed with correct polarity at phase detector output (V_P)

Frequency Acquisition

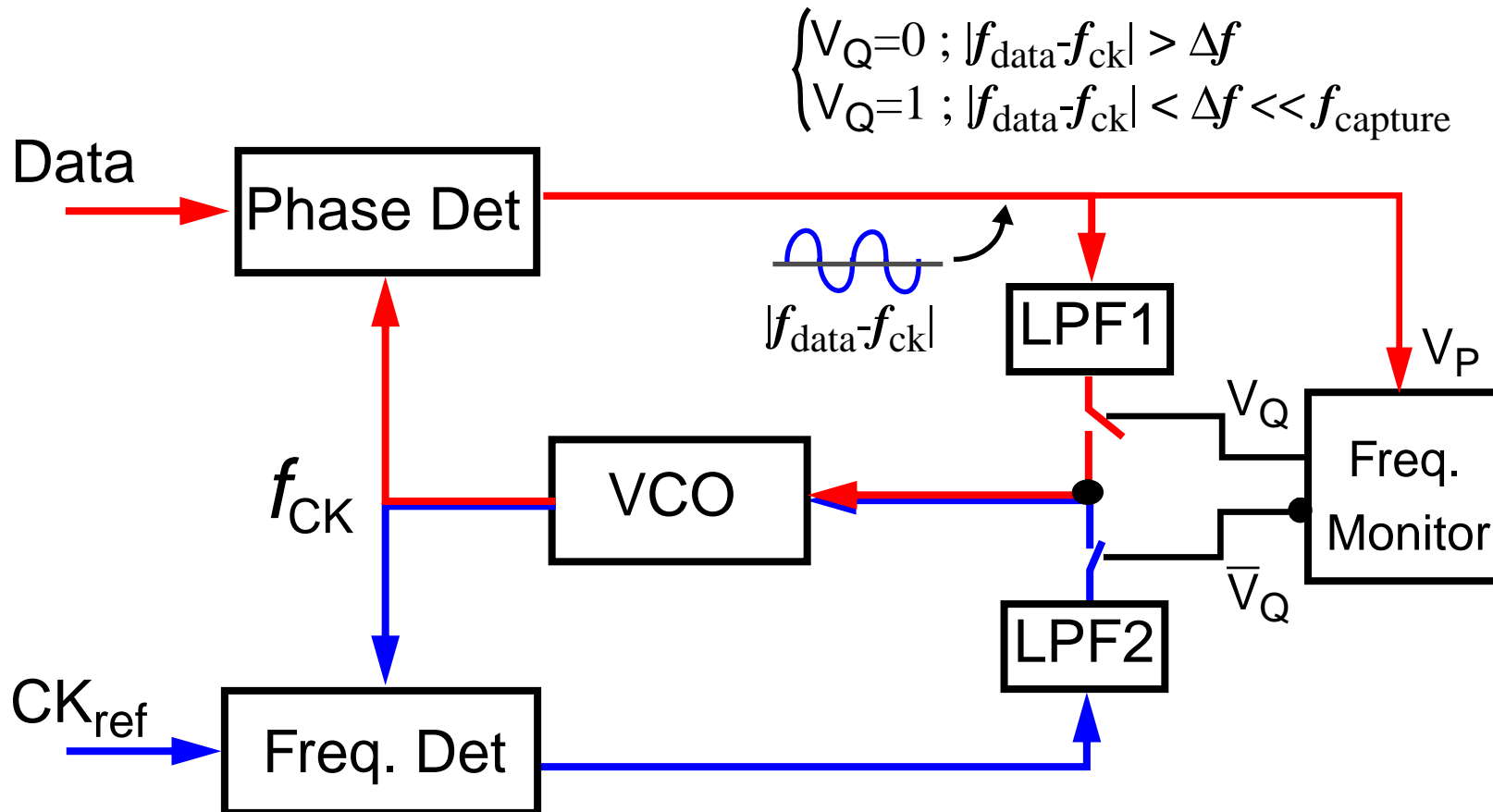
- A frequency acquisition aid solves the small capture range problem of the data-recovery phase detector
 - The frequency acquisition circuit sets the proper oscillation frequency before phase locking starts




Frequency Monitor

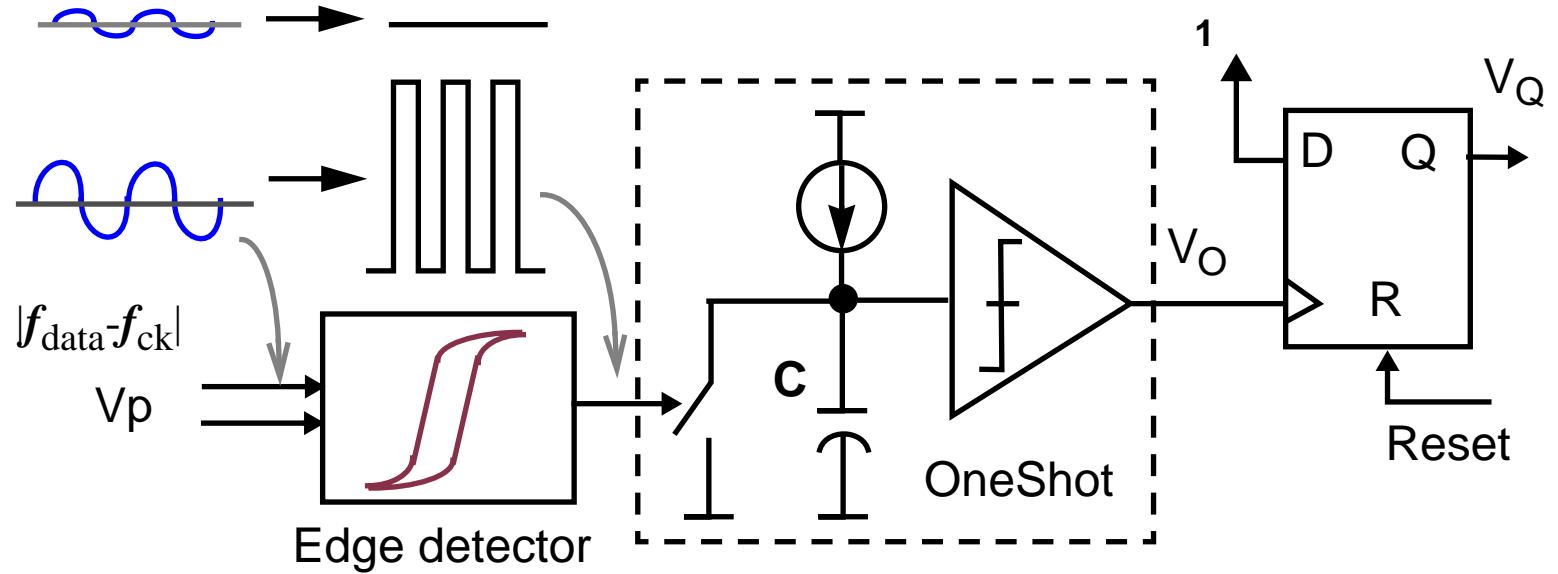

Top Level Architecture

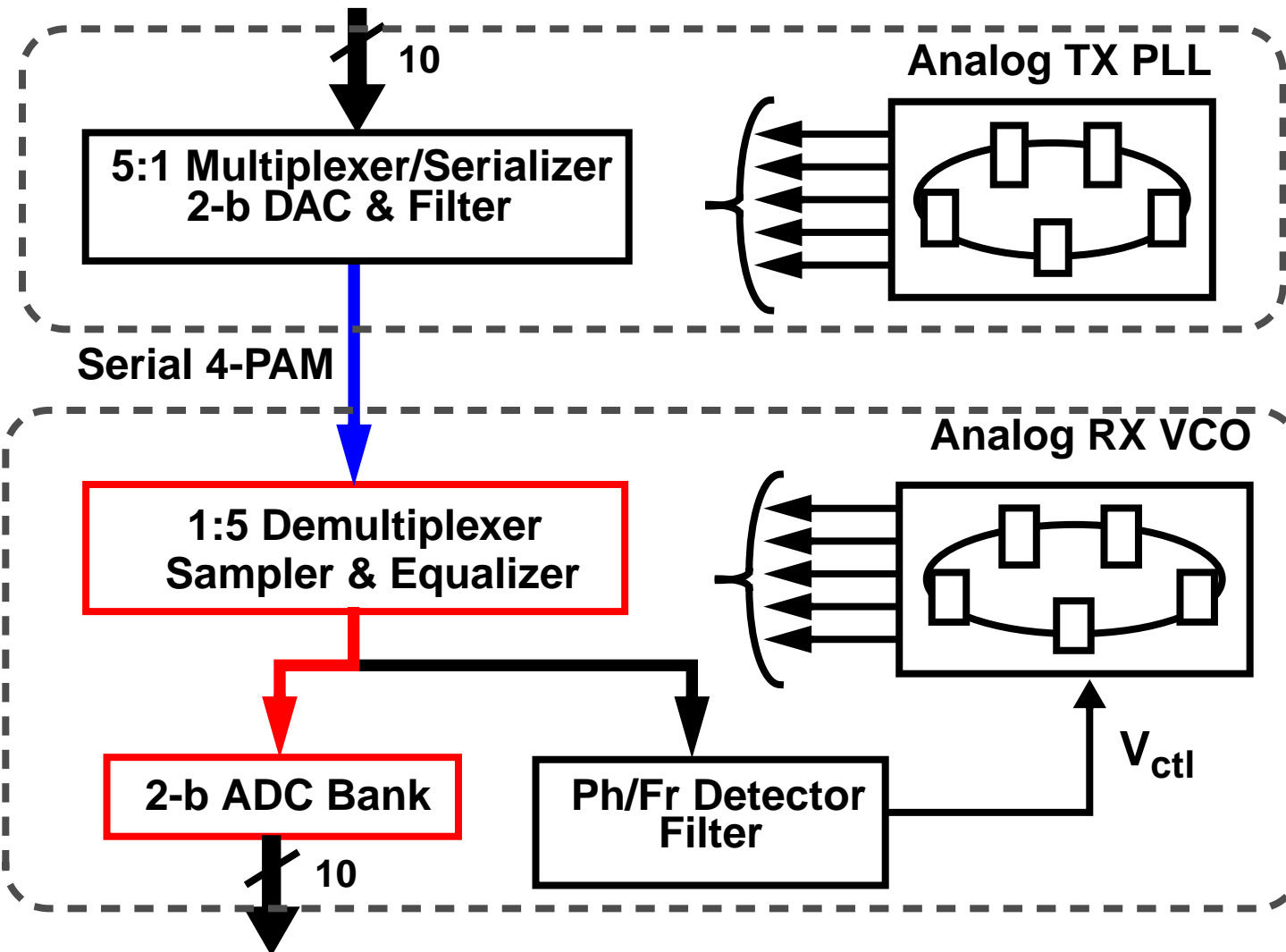

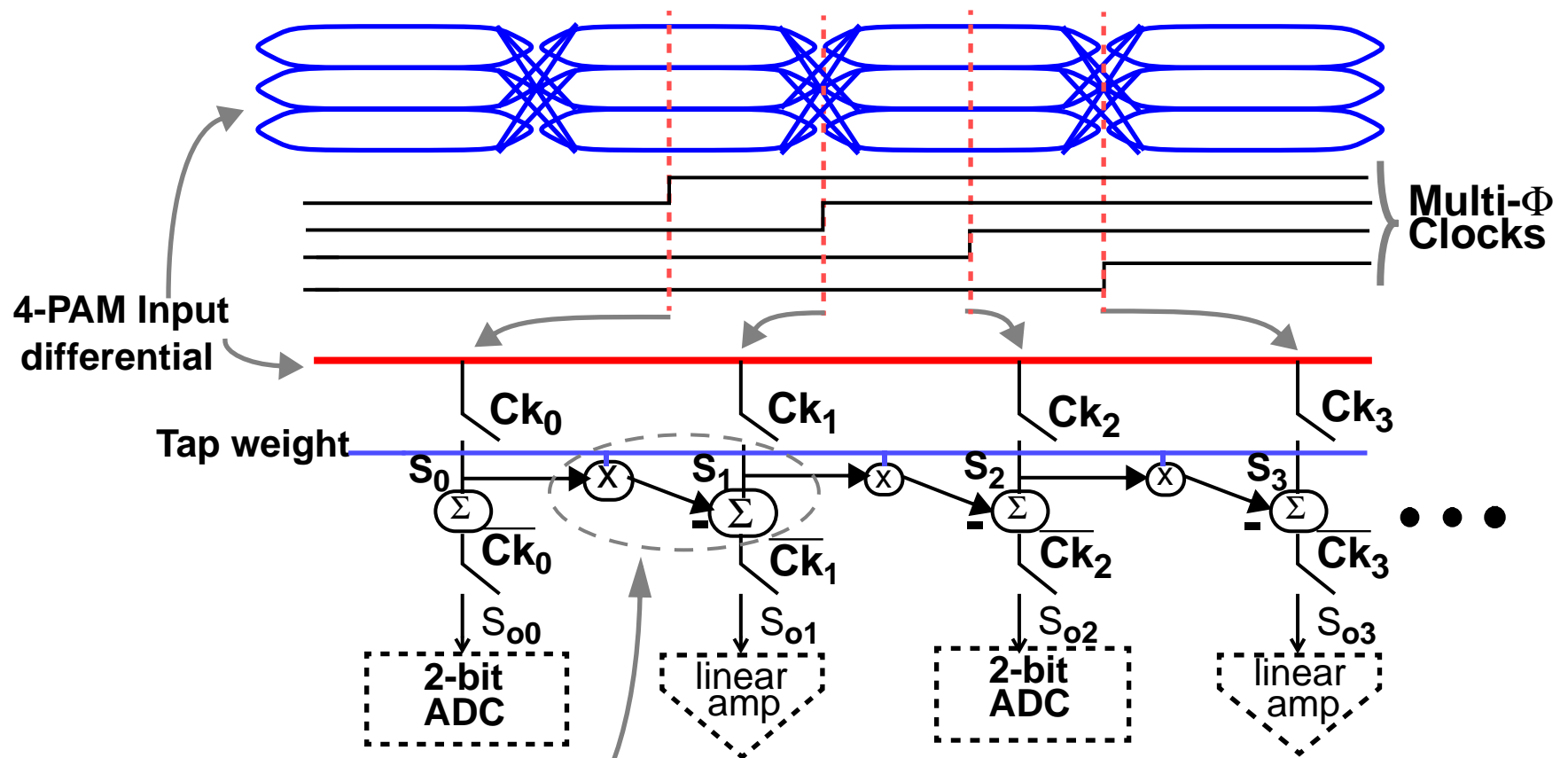1:5 Demultiplexing Samplers and Equalizers



(1-tap Equalizer: $S_{01} = S_1 - \alpha \cdot S_0$)


- 5 Samplers for the symbol centers and 5 samplers for transitions (x2 oversampling).
- Each equalizer uses the present and half a symbol earlier sample (half symbol spaced)

Half-symbol-Spaced 1-tap Equalizer

$$I_{O1} = I_1 - \alpha * I_0$$





$$S_{O1} = S_1 - \alpha * S_0$$

Analog 1-tap equalizer

 


- Equalization function should be performed very fast
 - Subtraction is done by summing the currents, which are proportional to the sampled values with opposite polarity.
- Differential pairs should have a large linear range for proper operation of analog equalization.

Input Preamplifier

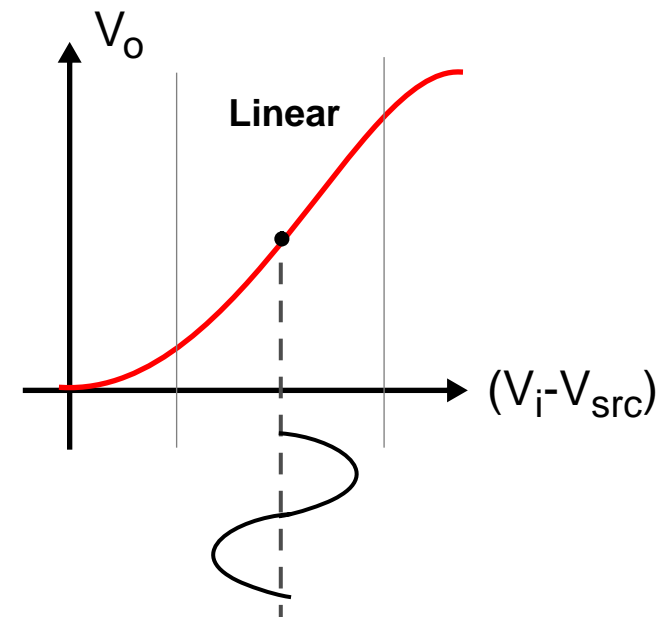 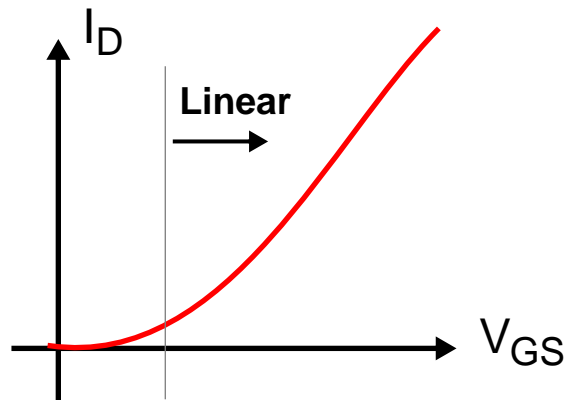 


- Short-channel MOS has a linear I_D - V_{GS} characteristic in saturation region
- “ V_{src} ” should be set such that V_o - V_i is linear for all values of V_i .

Differential 4-PAM Level detection

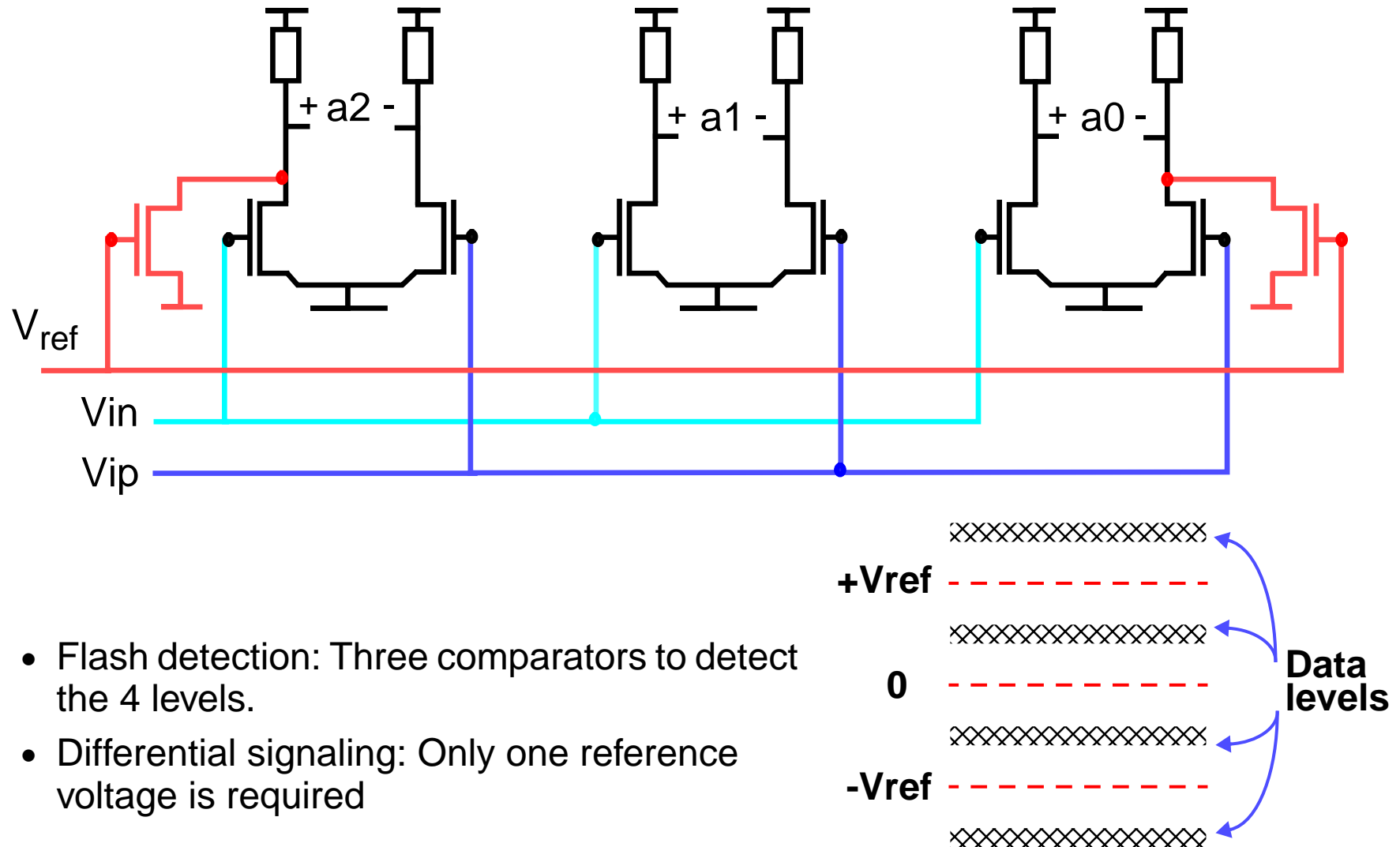




Input 2-bit ADC

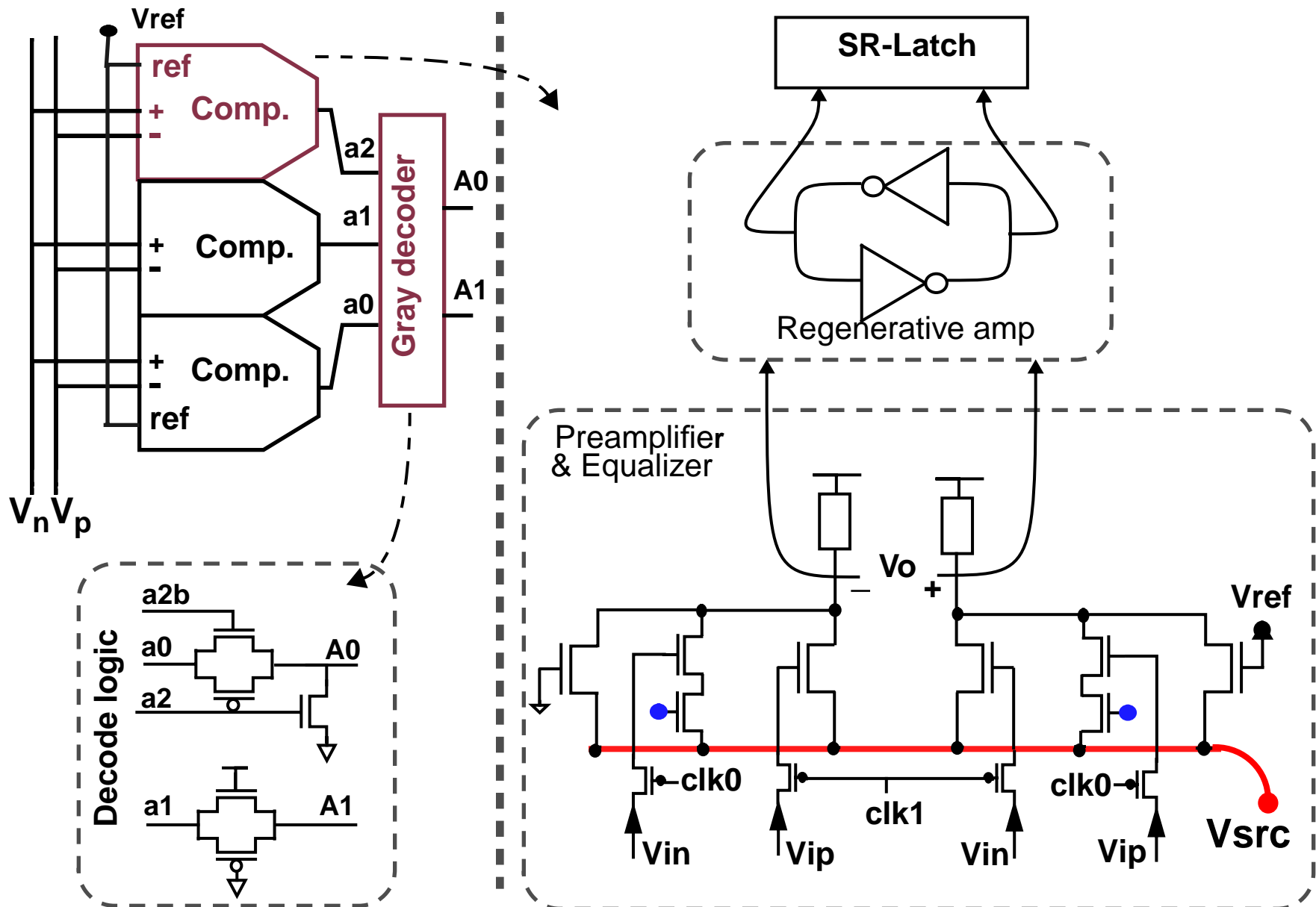

Outline




- Challenges
- System Architecture
- Implementation
- Test Results***
- Conclusion

Modeling The Cable

   


- SPICE models for skin effect are not ideal, need a better model:
 - Directly measure the cable impulse response (time domain)
 - Convolve it with the transmitted symbols

Simulated Eye Diagrams

   

- (a) Eye diagram after cable
(Without pre-emphasis)
- (b) Eye diagram after cable
(With pre-emphasis)
- (c) Eye diagram after cable
(With pre-emphasis/equalization)




0.35- μm Transmitter Die Photo

 

Total die area: 2mm x 1.5mm

4-PAM FIR transmitter: 0.8mm x 0.3mm

Measured Eye Diagrams

 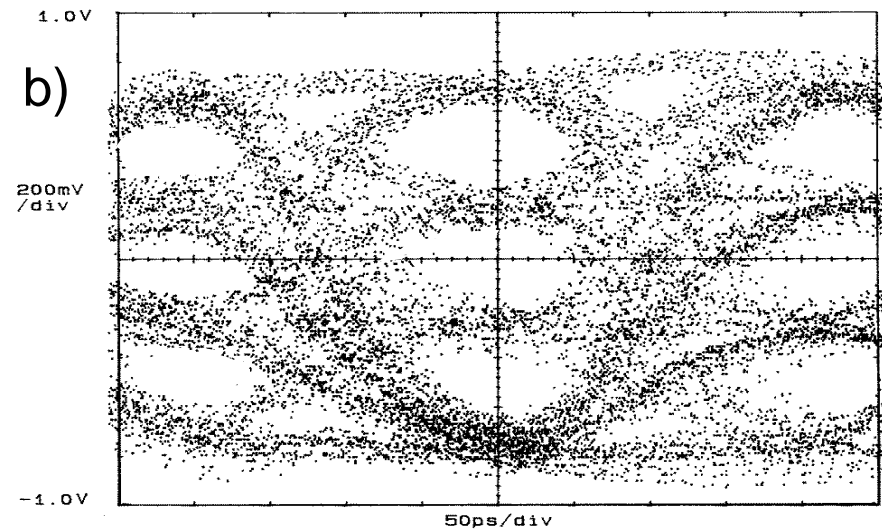 

- (a) 10Gb/s eye diagram at source
(No pre-emphasis)
- (b) 10Gb/s eye diagram after the cable
(With Pre-emphasis)
- (c) 8Gb/s Eye diagram after the cable
(With pre-emphasis)

0.35- μ m Transmitter Performance

Transmitter Data Rate	Eye Height	Eye Width
10Gb/s, 10meter, W/ Pre-emphasis	200mV	90ps - 70ps
10Gb/s, 10meter, No Pre-emphasis	0	0
8Gb/s, 10meter, W/ Pre-emphasis	350mV	110ps - 90ps
8Gb/s, 10meter, No Pre-emphasis	< 60mV	< 50ps


Transmitter Output Jitter:

Peak to peak	32ps
RMS	8ps

Power @ 10Gb/s (5Gsymb/s):

Analog	0.7watts
Output Driver	0.5watts
Sync/Logic	0.3watts
<hr/>	
Total	1.5watts

0.3- μm Full Transceiver Die Photo

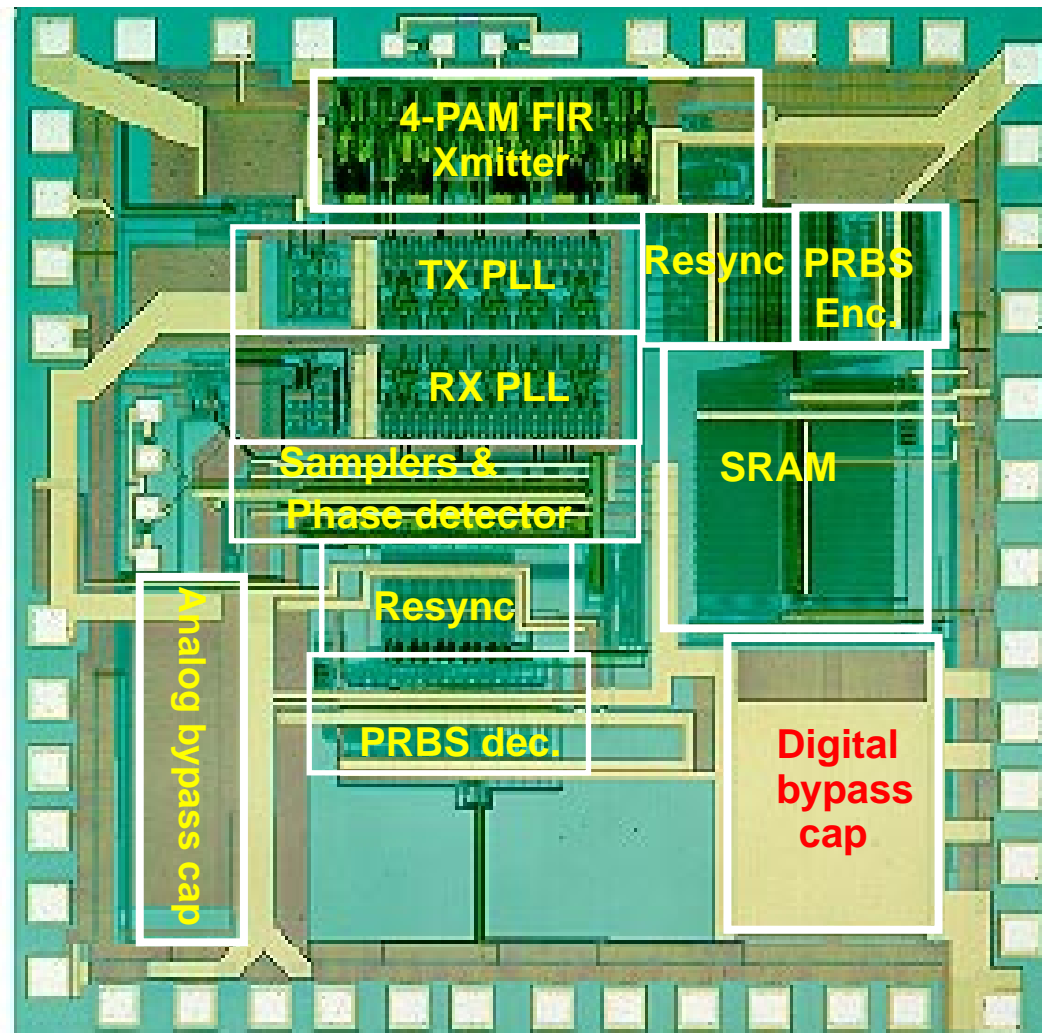

Total die area: 2mm x 2mm


Total receiver data recovery section: 0.85mm x 0.43mm

0.3- μ m Transceiver Performance

Maximum link speed	8Gbps @ 3V
Transmitter output Jitter @ 8Gbps	11ps (peak-peak), 2ps (rms)
Receiver PLL Jitter @8Gbps	28ps (peak-peak), 4ps (rms)
Receiver PLL dynamics	BW > 30MHz, Ph.m. > 48°
Receiver PLL capture range	~ 20MHz
Min. input swing to capture lock	\pm 400mV (diff.)
Min. input swing to maintain lock	\pm 300mV (diff.)

Power 8Gb/s, 3V	Analog: 750mW	4-PAM driver: 220mW	Other: 130mW	Total: 1.1W
--------------------	------------------	------------------------	-----------------	----------------

BER Measurements

 

→ At 8Gbps: BER $\sim 10^{-7}$, Window = 50ps

(almost no improvement with input equalizer)

→ At 6Gbps: BER $\sim 10^{-14}$, Window = 150ps

(30ps improvement with input equalizer)

- Possible factors for lower BER at high speeds:
 - **Line Reflection:** Bad on-chip terminations, package/bondwire
 - **EMI** from neighboring high-speed bondwires

Contributions


- A solution for multi-Gbps transmission over bandwidth-limited cables in standard CMOS technology:
 - Transmitter:
 - A high-speed 4-PAM DAC design to reduce the symbol rate to half (v.s. 2-PAM).
 - A FIR preshaping filter to perform at multi-Gbps rates with very low complexity.
 - A control circuit to optimize the width of the transmitted symbols.
 - Receiver:
 - An analog FIR equalizer effective up to multi-GHz ranges in CMOS technology.
 - A new proportional data-recovery phase detector for detecting 4-PAM serial data.
 - A new frequency-acquisition technique for data-recovery PLLs.
- A 4-PAM transceiver capable of data transmission up to 8 Gbps over 10-m copper cable with BW~1GHz in 0.3- μ m CMOS technology.

Acknowledgments


Future Work

- Use higher-level N -PAM modulation
 - Challenge: Very fast ADCs and DACs with higher resolution.
 - Explore general methods of N -PAM data recovery.
- Advanced communication methods for narrow-band channels:
 - Channel eigen function as transmission symbol.
 - Maximum likelihood detection (ML)
 - Multi-Carrier techniques (e.g DMT in ADSL)
 - Use coding methods to reduce BER.

Frequency Monitor

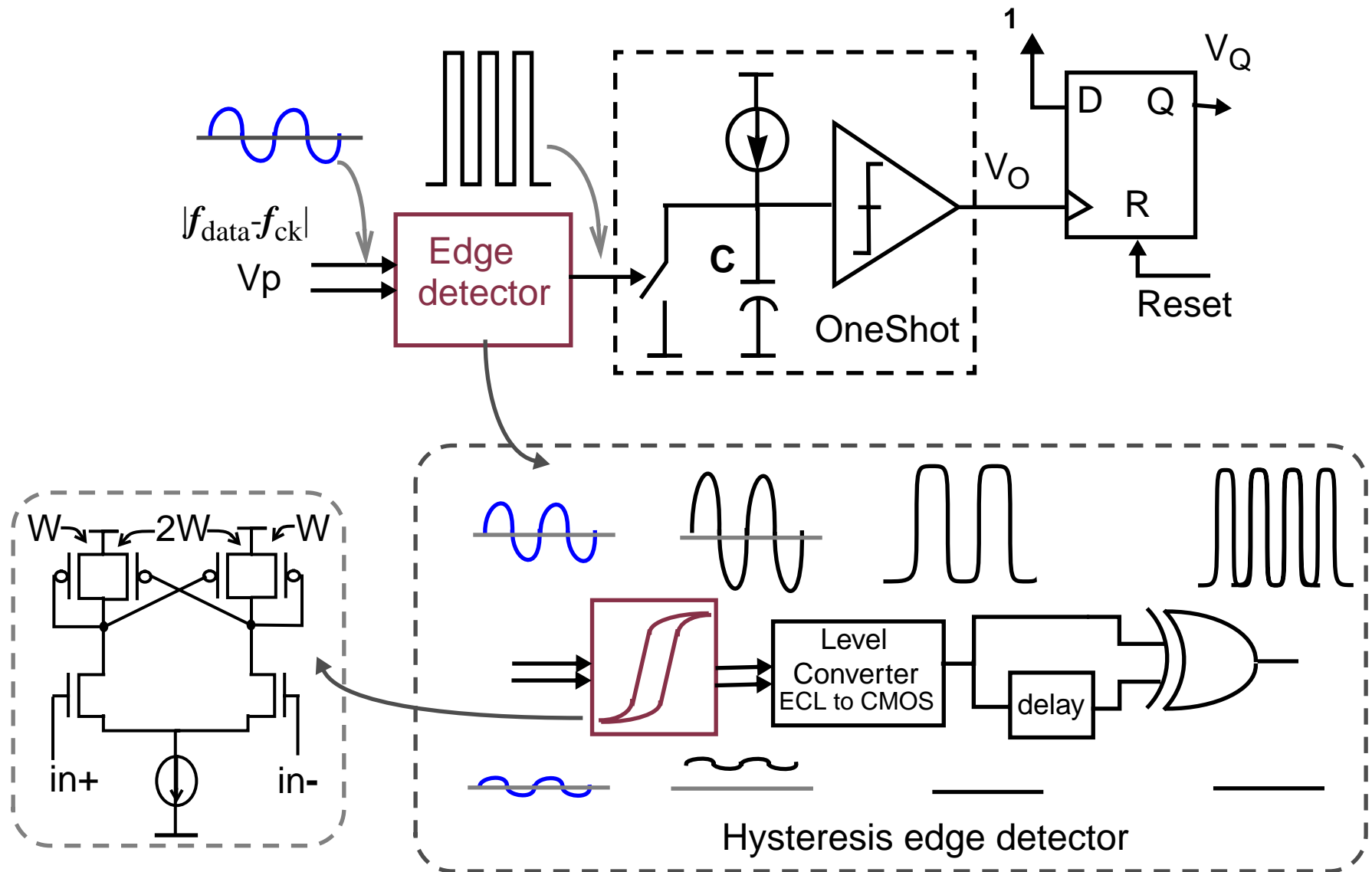

Analog Supply Drop

 

- The on-chip VCOs speed was limited to 800MHz (8Gbps) due to analog supply drop
 - Analog supply traces has $\sim 1.8\Omega$ resistance in series.
 - Only one pin for “Vdda” or “Gnda”
 - 250mA analog supply current at 8Gbps => $\sim 0.45V$ drop on analog supply!