

# A 5GHz, 32mW CMOS Frequency Synthesizer with an Injection–Locked Frequency Divider

*Hamid Rategh, Hirad Samavati, Thomas Lee*

# OUTLINE

---

- motivation
- introduction
- synthesizer architecture
- synthesizer building blocks
  - injection–locked frequency divider (**ILFD**)
  - voltage–controlled oscillator (VCO)
  - prescaler
  - charge pump and loop–filter
- summary
- conclusion


# MOTIVATION

- large demand on wideband wireless LAN systems
  - 20+Mb/s data rate
  - low cost
  - low power
- new released frequency band
  - unlicensed national information infrastructure (U–NII) band


# GOAL

- design a 5GHz frequency synthesizer for a U–NII band wireless–LAN receiver (HIPERLAN compatible)
- implement in CMOS
- minimize power consumption

## FREQUENCY OF OPERATION

 


# RECEIVER ARCHITECTURE

 

- $f_{RF} = 5.15\text{--}5.35\text{GHz}$
- $f_{LO} = \frac{16}{17}f_{RF}$


\* H. Samavati et al., “A 12.4mW CMOS Front–End for a 5GHz Wireless–LAN Receiver”, 1999 Symposium of VLSI Circuits, Session 9.2.

# INTEGER-N FREQUENCY SYNTHESIZER

 


- $f_{out} = M \times f_{ref}$
- $M = M_o + S$   
 $S = 0, 1, 2, \dots, 7$

# PULSE SWALLOW FREQUENCY DIVIDER

 


- one output cycle =  
$$(N + 1)S + (P - S)N = PN + S \text{ input cycles.}$$
- $f_{in} = (PN + S) \times f_{out}$
- $M = PN + S = M_o + S$

# PROPOSED ARCHITECTURE

 


# ILFD SIMPLIFIED PICTURE

 

- oscillator feedback model with perturbation
- oscillation conditions should be satisfied in the presence of the incident signal
 
# VOLTAGE-CONTROLLED DIFFERENTIAL ILFD

- $0.24\mu\text{m}$  CMOS
- $\text{Vdd}=1.5\text{V}$
- $I_{\text{bias}}=300\mu\text{A}$
- $f_o=2.25\text{GHz}$
- $f_i=4.5\text{GHz}$





## INDUCTOR DESIGN (ILFD)

---

- maximum locking range  $\Rightarrow$  maximize  $L$
- minimum power consumption  $\Rightarrow$  maximize  $LQ$

# INDUCTOR DESIGN

  

- design parameters:

- $w$ : metal width
- $s$ : metal spacing
- $OD$ : outer dimension
- $n$ : number of turns

## INDUCTOR DESIGN (ILFD)

---


- in planar spiral inductors maximizing  $L$  does not maximize  $LQ$




maximize  $L$  for a given  $LQ$
 
# VCDILFD FREQUENCY RANGE

- $0.24\mu\text{m}$  CMOS
- $\text{Vdd}=1.5\text{V}$
- $I_{\text{bias}}=300\mu\text{A}$



# TRACKING ILFD

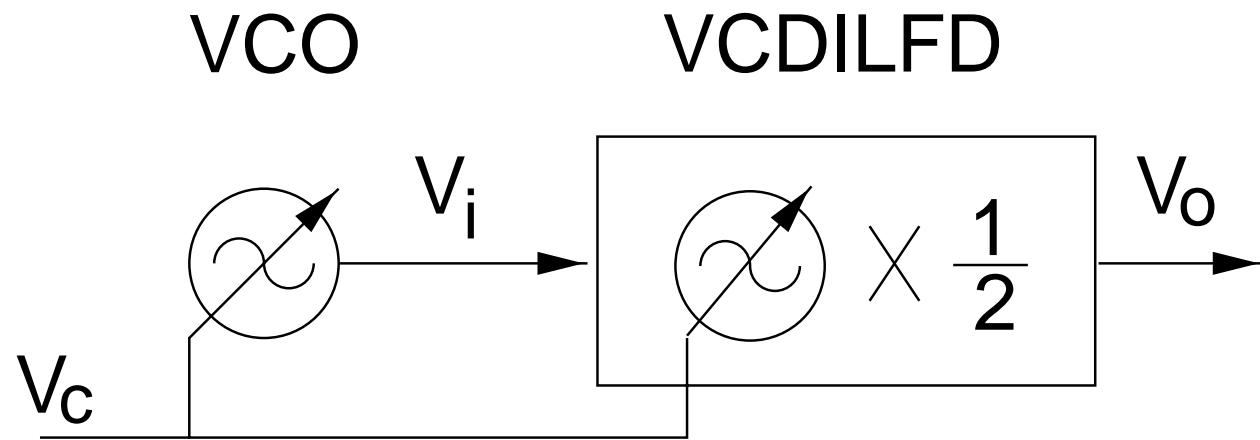

- locking range extension

## ILFD SUMMARY

---

maximum frequency of operation	5GHz
output frequency tuning	110MHz $\approx$ 5%
input-referred locking range	450MHz $\approx$ 10% @ 0.7mW 900MHz $\approx$ 20% @ 1.0mW
technology	0.24μm CMOS
die area	0.186mm <sup>2</sup>

---


### *flip-flop-based divider*

0.24μm CMOS (simulation)	7mW @ 5GHz
0.1μm CMOS	2.6mW @ 5GHz


(Razavi *et al.*, JSSC Vol. 30, No.2, pp 101–109, Feb. 1995)
 
# VOLTAGE-CONTROLLED OSCILLATOR

- $0.24\mu\text{m}$  CMOS
- $\text{Vdd}=1.5\text{V}$
- $I_{\text{bias}}=2.0\text{mA}$
- $f_o=4.85\text{GHz}$



# VARACTOR

 

- accumulation mode MOS capacitor
  - large quality factor ( $> 60$  @ 5GHz)
  - flat-band voltage  $\approx$  zero

\* A. S. Porret et al., CICC Digest, pp 641-644, 1999.

\* T. Soorapanth et al., Symposium on VLSI Circuits Digest, pp 32–33, 1998.


# INDUCTOR DESIGN (VCO)

---


- maximum  $Q \Rightarrow$  minimum inductor noise
- if inductors are not the main source of noise, maximum  $LQ \Rightarrow$ 
  - maximum oscillation amplitude for a given bias current
  - minimum phase noise
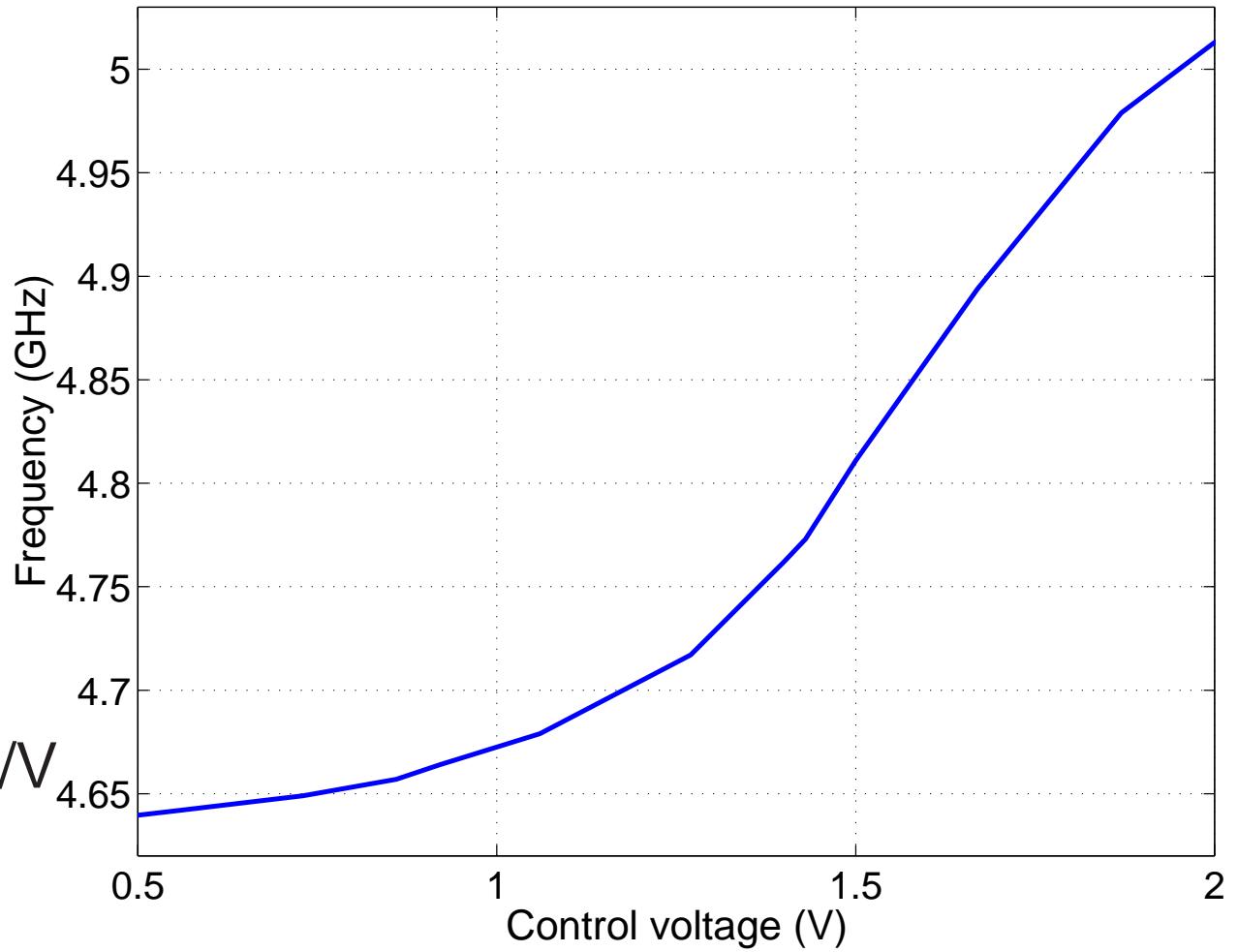
# VCO FREQUENCY TUNING

- $0.24\mu\text{m}$  CMOS
- $\text{Vdd} = 1.5\text{V}$
- $I_{\text{bias}} = 2.0\text{mA}$
- $\Delta f = 370\text{MHz}$   
 $\approx 7.7\%$
- $\Delta V_c = 1.5\text{V}$
- $(\frac{df}{dv})_{\text{max}} = 500\text{MHz/V}$




# PRESCALER

 

- divide by 22/23
- $N = 2^4 + S_1 \cdot 2^0 + S_2 \cdot 2^1 + S_3 \cdot 2^2$


# PRESCALER (ZERO GATE DELAY)

 

- $N = 2^4 + S_1 \cdot 2^0 + S_2 \cdot 2^1 + S_3 \cdot 2^2$
- $T_{clk} = 400\text{ps}$
- $D_{FO4} = 160\text{ps}$  (Slow process + high temperature)

# PRESCALER (NON ZERO GATE DELAY)

---

 

- problem: gate delays add
- solution:
  - make gates faster  $\Rightarrow$  burn more power
  - use quadrature outputs to generate swallow commands

# CHARGE PUMP AND LOOP-FILTER

- $I=50\mu A$


- $R1=47k\Omega$

- $R3=8k\Omega$

- $C1=30pF$

- $C2=3.3pF$


- $C3=2pF$

 
 
# LOOP-FILTER NOISE

---


- $L = -107 \text{ dBc/Hz}$   
@ 1MHz
- $L = -137 \text{ dBc/Hz}$   
@ 10MHz
- $L = -145 \text{ dBc/Hz}$   
@ 22MHz


 
# PLL PHASE NOISE


---

- $L = -101 \text{ dBc/Hz}$   
@ 1MHz
- $L = -127.5 \text{ dBc/Hz}$   
@ 22MHz


 
# SYNTHESIZER CHIP MICROGRAPH

- $0.24\mu\text{m}$  CMOS
- area= $1.6\text{mm}^2$   
 $(1\text{mm} \times 1.6\text{mm})$



# SUMMARY

Synthesized frequencies	4.840–4.994GHz
Reference frequency	11MHz
LO spacing	22MHz
Spurs	$\leq -45\text{dBc}$ @ $f_{ref}$ , $\leq -54\text{dBc}$ @ $2 \times f_{ref}$
Phase noise	-101dBc/Hz @ 1MHz
VCO power	3.0mW
VCDILFD power	1.2mW
Prescaler power	25.4mW
Total power	32mW
Supply voltage	2.0V (1.5V for VCO & VCDILFD)
Die area	1.6mm <sup>2</sup>
Technology	0.24 $\mu$ m CMOS

# COMPARISON

reference	$f$ (GHz)	power	L	FM	comment
Parker, JSSC 98	1.6	90mW	$0.6\mu\text{m}$	10.6	integer-N
Craninckx, ISSCC 98	1.8	51mW	$0.4\mu\text{m}$	14.1	fractional-N
Shahani, JSSC 98	1.6	36mW	$0.5\mu\text{m}$	22.2	dividerless
This work	5.0	32mW	$0.24\mu\text{m}$	37.5	integer-N

- $\text{FM} = \frac{f \times L}{\text{power}}$

## CONCLUSION

---

- A 5GHz frequency synthesizer is fully integrated in  $0.24\mu\text{m}$  CMOS
- power consumption is reduced by
  - employing a voltage-controlled ILFD
  - optimizing spiral inductors for the VCO and ILFD
  - taking advantage of quadrature outputs in the prescaler
- loop-filter noise is kept small by using reasonably small resistors
- low spurious side bands are achieved by
  - using a semi-differential charge pump
  - designing a fourth-order loop

## ACKNOWLEDGMENTS

---

M. Hershenson

S. Mohan

T. Soorapanth

National Semiconductor

Stanford Graduate Fellowship Program